

**University of Southern California**

**Viterbi School of Engineering**

**EE577A**  
**VLSI System Design**


**Data Path Design**

**References: Professor Massoud Pedram's lecture slides,  
books listed in the syllabus, and online resources**

**Shahin Nazarian**

**Spring 2013**

# Single-Bit Addition

 


## Half Adder

$$S = A \oplus B$$

$$C_{\text{out}} = A \cdot B$$

A	B	$C_{\text{out}}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

## Full Adder

 

$$S = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C) = AB + (A + B)C$$

$$= AB + (A \oplus B)C$$

A	B	C	$C_{\text{out}}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- For a full adder, define what happens to carries
  - **Generate:**  $C_{out} = 1$  independent of  $C$ 
$$G = A \cdot B$$
  - **Propagate:**  $C_{out} = C$ 
$$P = A \oplus B$$
  - **Kill:**  $C_{out} = 0$  independent of  $C$ 
$$K = \bar{A} \cdot \bar{B}$$
  - **Note that**


$$\bar{P} = A \cdot B + \bar{A} \cdot \bar{B} = G + K$$

# Full Adder Design I

- Brute force implementation from equations

$$S = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C)$$

 


# Full Adder Design II

- Factor  $S$  in terms of  $C_{out}$


$$S = ABC + (A + B + C)\overline{C_{out}}$$

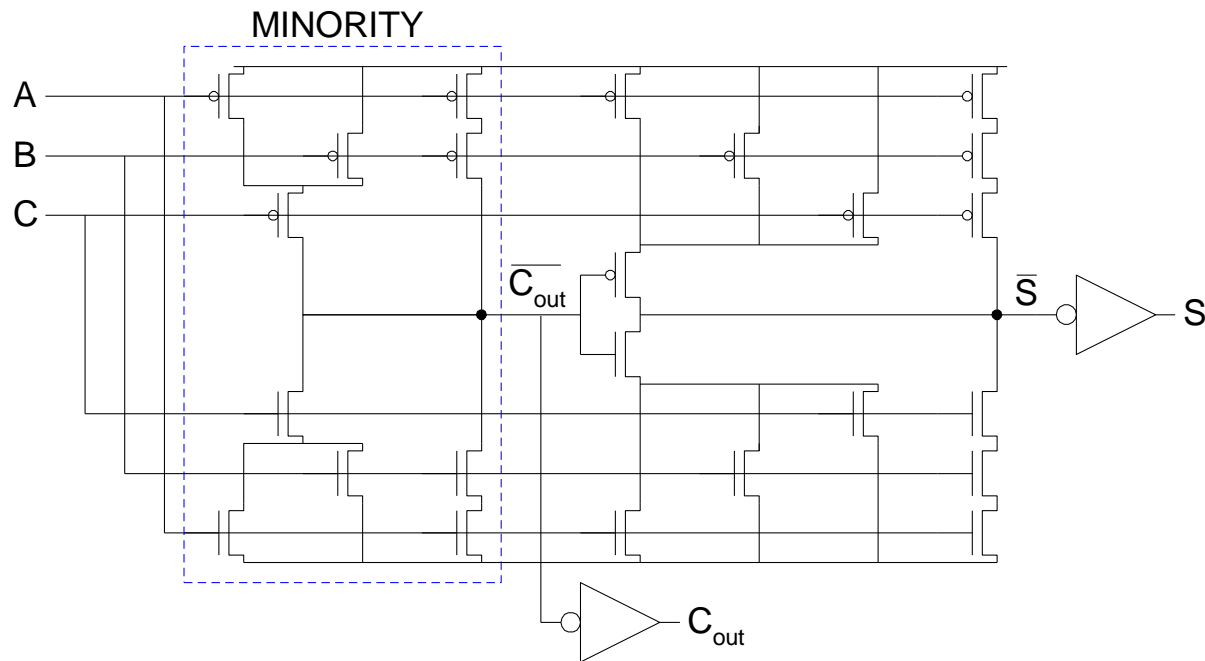- Critical path is usually  $C$  to  $C_{out}$  in a ripple adder



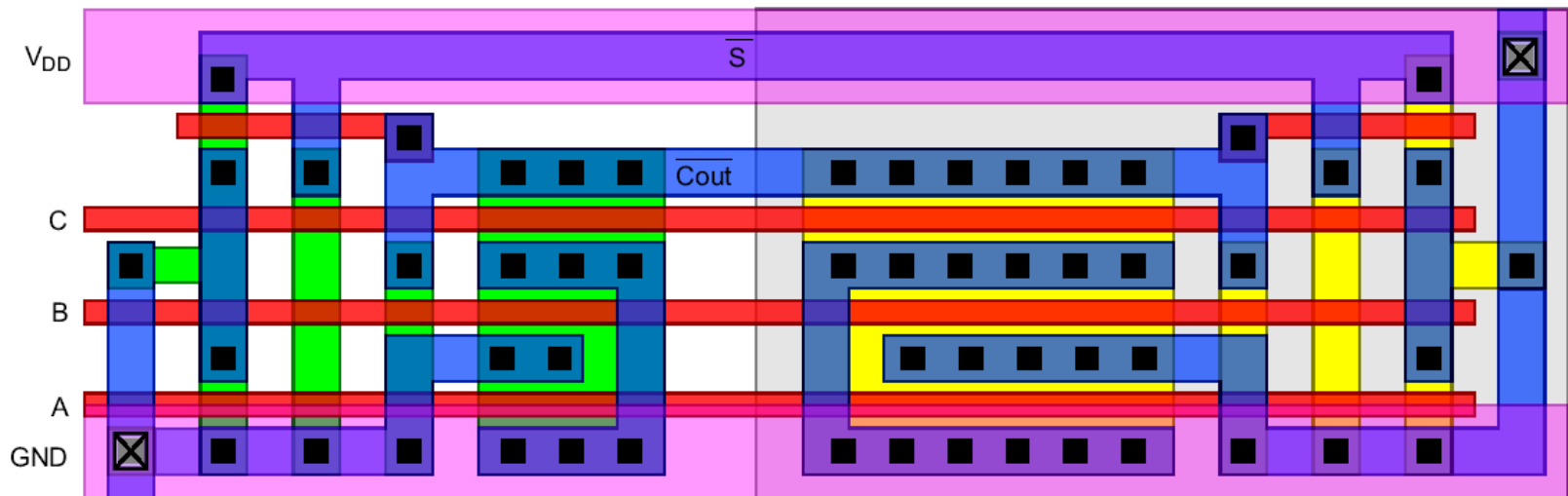
# Layout

- Clever layout circumvents usual line of diffusion
  - Use wide transistors on critical path
  - Eliminate output inverters



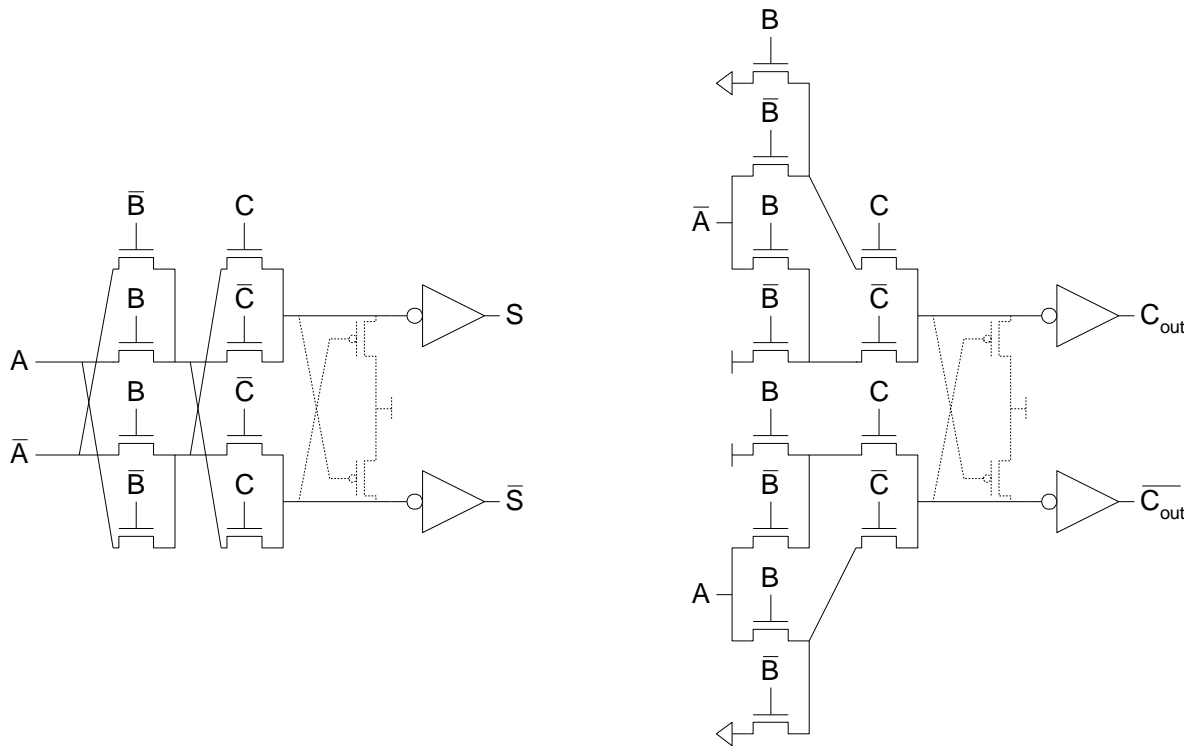
# Full Adder Design III

- Complementary Pass Transistor Logic (CPL)
  - Slightly faster, but more area


 
# Carry Propagate Adders (CPA)

- N-bit adder called CPA
  - Each sum bit depends on all previous carries
  - How do we compute all these carries quickly?



$$\begin{array}{r} \textcircled{0}000\textcircled{0} \\ 1111 \\ +0000 \\ \hline 1111 \end{array}$$

Carry propagation example 1: The carry chain is 0 → 0 → 0 → 0 → 0. The final carry-out is 0.

$$\begin{array}{r} \textcircled{1}111\textcircled{1} \\ 1111 \\ +0000 \\ \hline 0000 \end{array}$$


Carry propagation example 2: The carry chain is 1 → 1 → 1 → 1 → 1. The final carry-out is 1.

carries  
 $A_{4...1}$   
 $B_{4...1}$   
 $S_{4...1}$



 
# Carry-Ripple Adder (CRA)

- Simplest design: cascade full adders
  - Critical path goes from  $C_{in}$  to  $C_{out}$
  - Design full adder to have fast carry delay


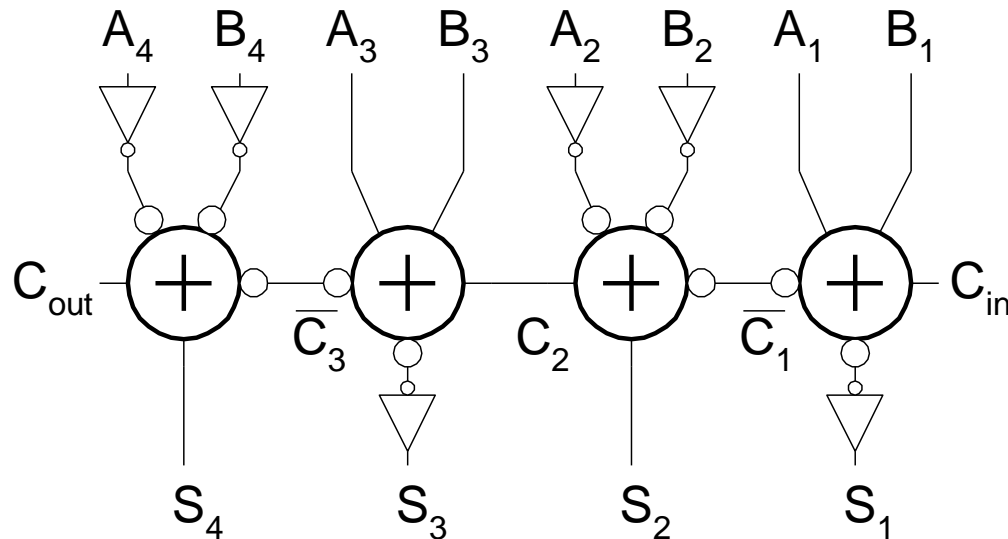
# Inversions

- Critical path passes through majority gate
  - Built from minority + inverter
  - Eliminate inverter and use inverting full adder



# Generate / Propagate

- Equations often factored into  $G$  and  $P$
- Generate and propagate for groups spanning  $i:j$  ( $j \leq i$ )

$$\forall k = i, i-1, \dots, j+1:$$

$$G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$$

$$P_{i:j} = P_{i:k} \cdot P_{k-1:j}$$

$$G_{i:j} \cdot P_{i:j} = 0$$

$$G_i \cdot P_i = 0$$

- Base case

$$G_{i:i} \equiv G_i = A_i B_i$$

$$P_{i:i} \equiv P_i = A_i \oplus B_i$$

$$G_{0:0} \equiv G_0 = C_{in}$$

$$P_{0:0} \equiv P_0 = 0$$

- Because the carry into bit  $i$  is the carry-out of bit  $i-1$ , which is:  $C_{i-1} = G_{i-1:0}$ , the sum is:  $S_i = P_i \oplus G_{i-1:0}$

# Comment on Calculating the Generate/Propagate Signals

- In some textbooks, you will find the following:

$$G_{i:i} \equiv G_i = A_i B_i$$

$$P_{i:i} \equiv P_i = A_i + B_i$$

$$G_i \cdot P_i \neq 0 \text{ and } G_{i:j} \cdot P_{i:j} \neq 0$$


- If you use these equations, then therefore, we must calculate the sum bit as follows:

$$S_i = P_i \oplus G_i \oplus G_{i-1:0}$$

- Expressions for  $G_{i:j}$  and  $P_{i:j}$  remain the same, including

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$


# Efficient Realization of XOR Gate

 

**XOR function:**

**If  $A=0$ , pass input B; Otherwise, invert input B**


# PG Logic

 

# CRA Revisited

$$\begin{aligned}
 C_i &= A_i B_i + (A_i + B_i) C_{i-1} \\
 &= A_i B_i + (A_i \oplus B_i) C_{i-1} \\
 &= G_i + P_i C_{i-1}
 \end{aligned}$$

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

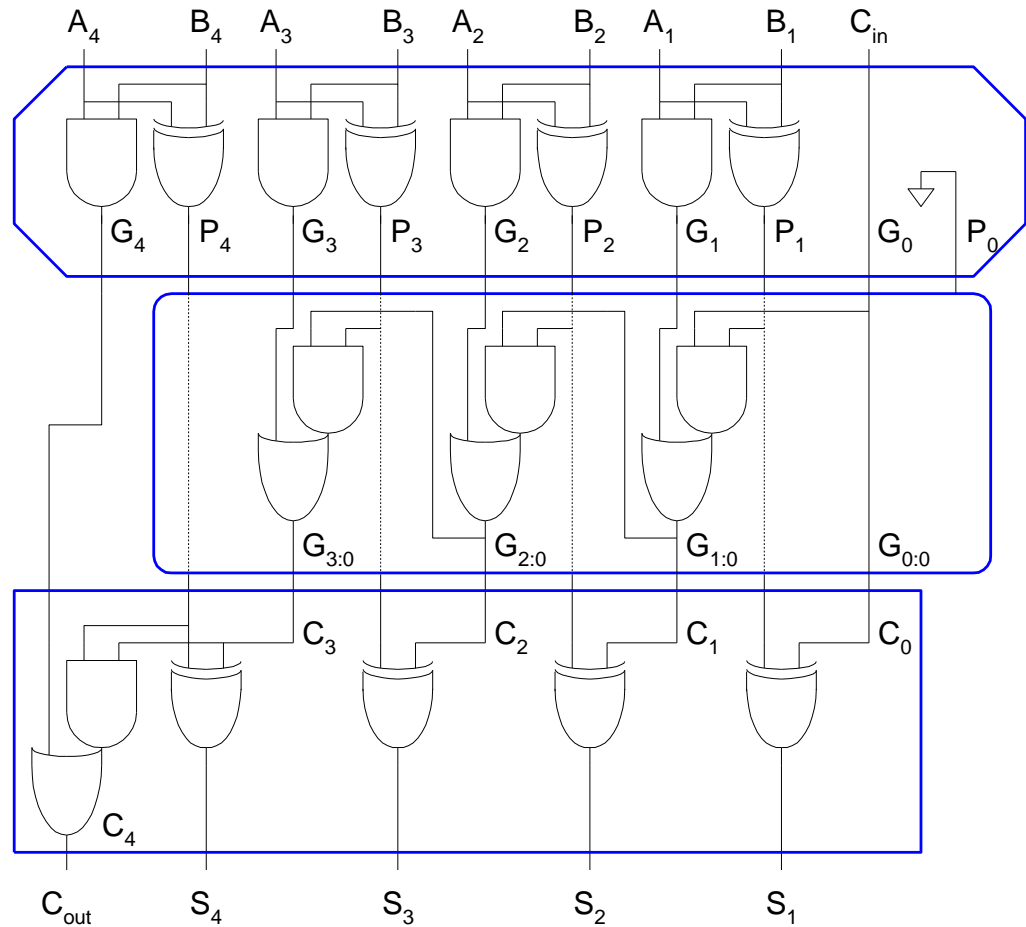

# CRA PG Diagram

- Adding two operands:  
 $A[1:16]$  and  $B[1:16]$
- The Bitwise PG Logic and Sum Logic blocks are not shown
- Gray cells contain only the group generate logic
- Final sum is computed as:


$$S_{16} = P_{16} \oplus G_{15:0} = P_{16} \oplus C_{15}$$

- Final carry-out is computed as:

$$C_{16} = G_{16:0} = G_{16} + P_{16}C_{15}$$

- The critical path delay from carry-in to sum bit is:

 
$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{\text{xor}}$$






# PG Diagram Notation





Black cell

 

Gray cell

 

Buffer

    


Notice that, for the Gray cell, vertical input line carries both  $G_{i:k}$  and  $P_{i:k}$  signals whereas the diagonal input line only provides the  $G_{k-1:j}$  signal

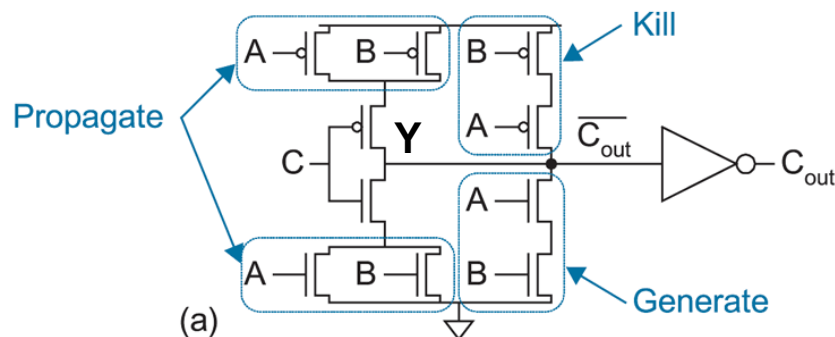
# Carry Chain Designs (Optional)

Recall that:


$$P = A \oplus B, \quad G = A \cdot B, \quad K = \bar{A} \cdot \bar{B}$$



Static Version

 

Dynamic Version

 

C	A, B	Y	G	K	C <sub>out</sub>
1	$A + B$	0	-	0	1
1	$\bar{A} \cdot \bar{B}$	float	0	1	0
0	$\bar{A} + \bar{B}$	1	0	-	0
0	$A \cdot B$	float	1	0	1


$$C_{out} = C_{in} \cdot (A + B) + G = MAJ(A, B, C_{in})$$

$$= C_{in} \cdot P + G$$

$$\bar{C}_{out} = \bar{C}_{in} \cdot (\bar{A} + \bar{B}) + K = MIN(A, B, C_{in})$$

$$= \bar{C}_{in} \cdot P + K$$


# Manchester Carry Chain (Optional)

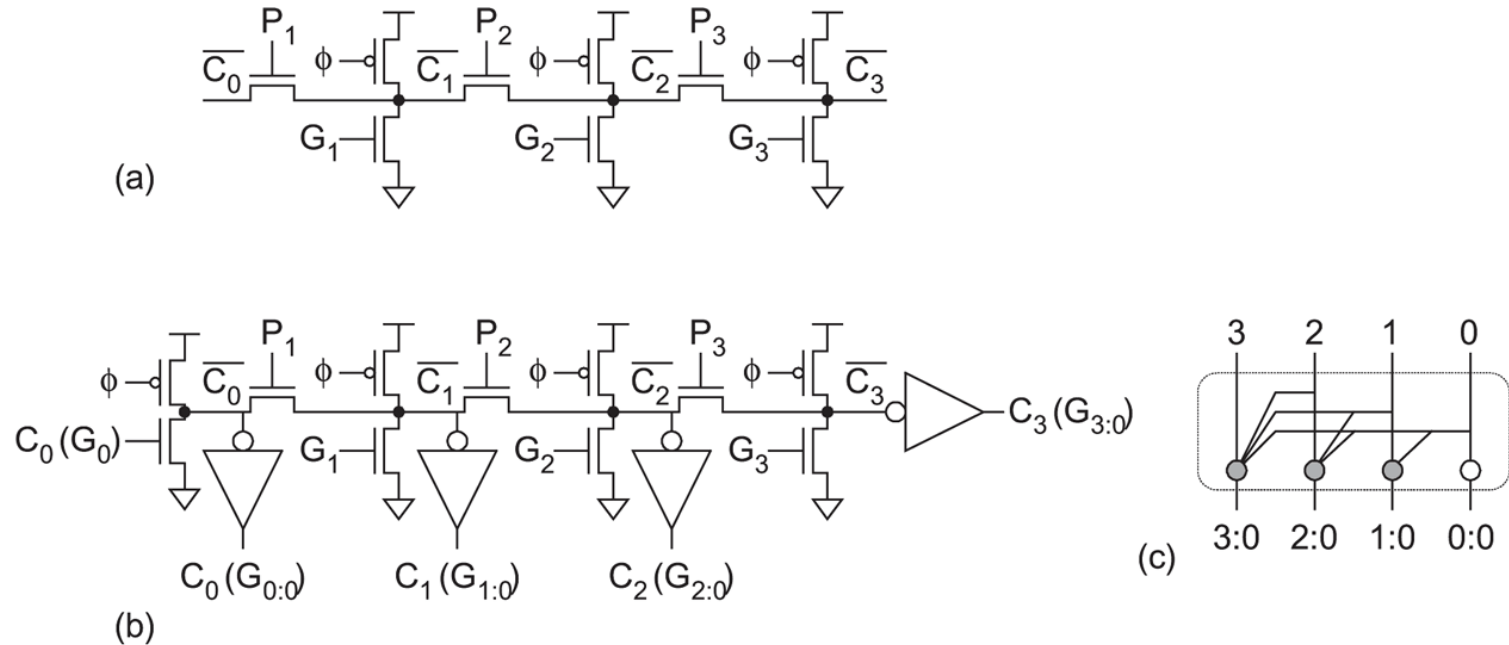

Manchester carry chains

One may also use the static version of Manchester Carry Chain (MCC)

# MCC Adder PG Network (Optional)

 


Manchester carry chain adder group PG network

- With valency- $n$  MCC stages i.e.,  $N=(n-1).k$  :

$$t_{mcca} = t_{pg} + kt_{mcc(n)} + t_{xor}$$
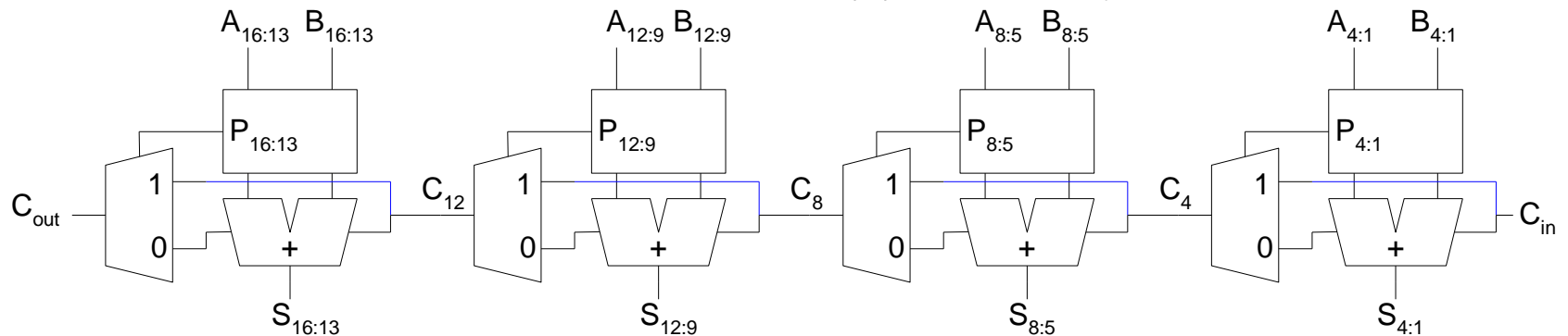
# Carry-Bypass Adder (CBA)

- Carry-bypass allows carry to skip over groups of  $n$  bits
  - Decision is based on the  $n$ -bit propagate signal
  - The bypass speeds up the addition because either the carry-in propagates through the bypass path, or the carry-in is (first killed and subsequently re-) generated in the chain. In both cases, the delay is smaller than the normal ripple carry adder



Example:  $n=4$


$$C_{12} = \bar{P}_{12:9} \cdot G_{12:9} + P_{12:9} \cdot C_8$$

$$\text{Since } G_{12:9} \subseteq \bar{P}_{12:9},$$

$$C_{12} = G_{12:9} + P_{12:9} \cdot C_8$$

This means that the MUX gate may be replaced with a simple AO gate


# CBA PG Diagram

 

For  $k$  groups of  $n$  bits each ( $N = k.n$ ) and replacing MUX's w/ AO gates:

$$t_{\text{skip}} = t_{pg} + 2(n-1)t_{AO} + (k-1)t_{mux} + t_{xor} = t_{pg} + (2n+k-3)t_{AO} + t_{xor}$$


# CBA w/ Variable Group Size

 

**Group sizes: (2,3,4,4,3)**

**Delay grows as  $O(\sqrt{N})$**

# CBA Manchester Stage (Optional)

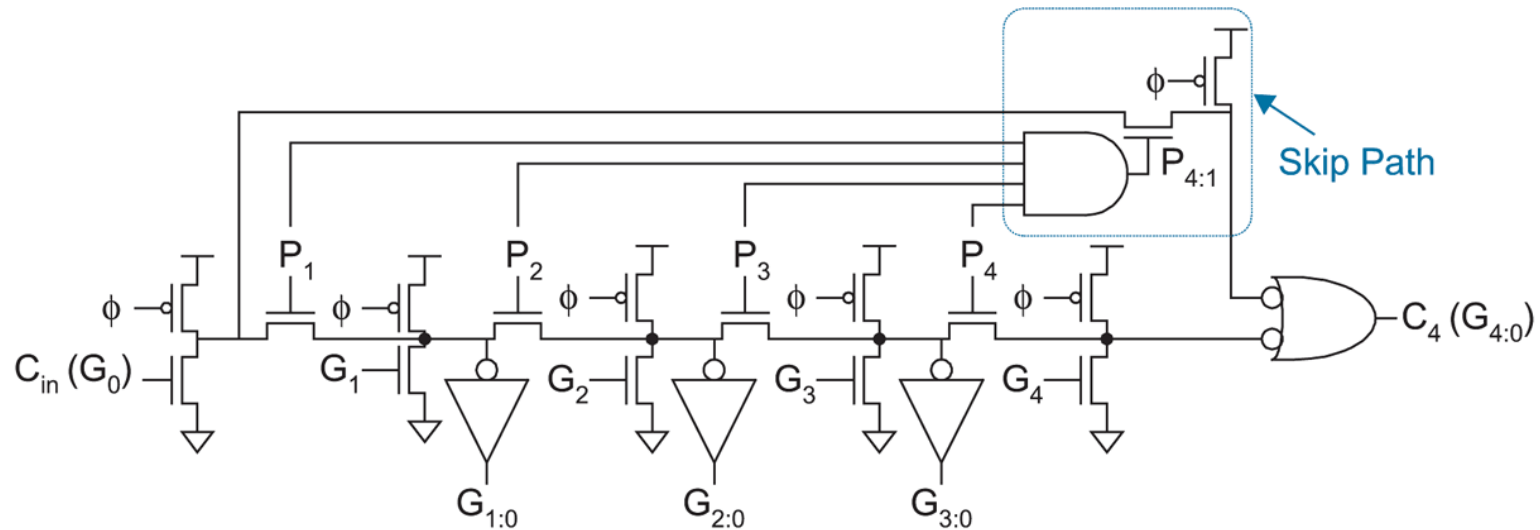


Carry-skip adder Manchester stage

**Skips across carry groups of 4 bits at a time**


 
# Carry-Lookahead Adder (CLA)


- Carry-lookahead adder computes  $G_{i:0}$  for many bits in parallel
- Uses higher-valency cells with more than two inputs


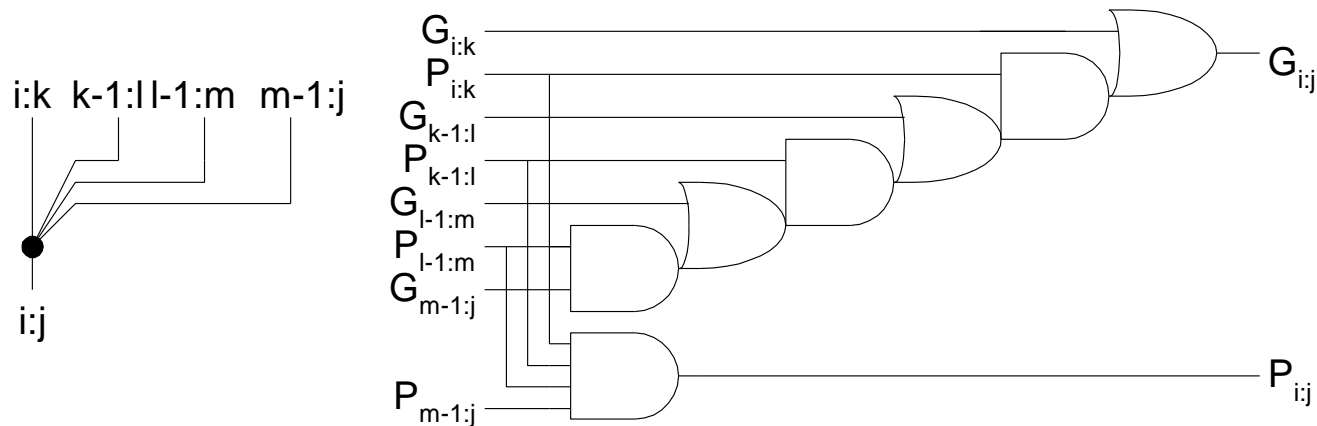
# Higher-Valency Group PG Cells


$$G_{i:j} = G_{i:k} + P_{i:k} \cdot (G_{k-1:l} + P_{k-1:l} \cdot (G_{l-1:m} + P_{l-1:m} \cdot G_{m-1:j}))$$

$$P_{i:j} = P_{i:k} \cdot P_{k-1:l} \cdot P_{l-1:m} \cdot P_{m-1:j}$$



**Valency-4 black cell**

# CLA PG Diagram

 


Carry-lookahead adder group PG network

- For  $k$  groups of  $n$ -bits each :

$$t_{\text{CLA}} = t_{pg} + t_{pg(n)} + \left[ (n-1) + (k-1) \right] t_{AO} + t_{\text{xor}}$$

# Improved CLA with MCCs (Optional)

 


- For  $k$  groups of  $n$ -bits each and valency- $n$  MCC blocks:

$$t_{\text{CLA+MCC}} = t_{pg} + t_{pg(n)} + (k-1)t_{AO} + t_{mcc(n)} + t_{\text{xor}}$$
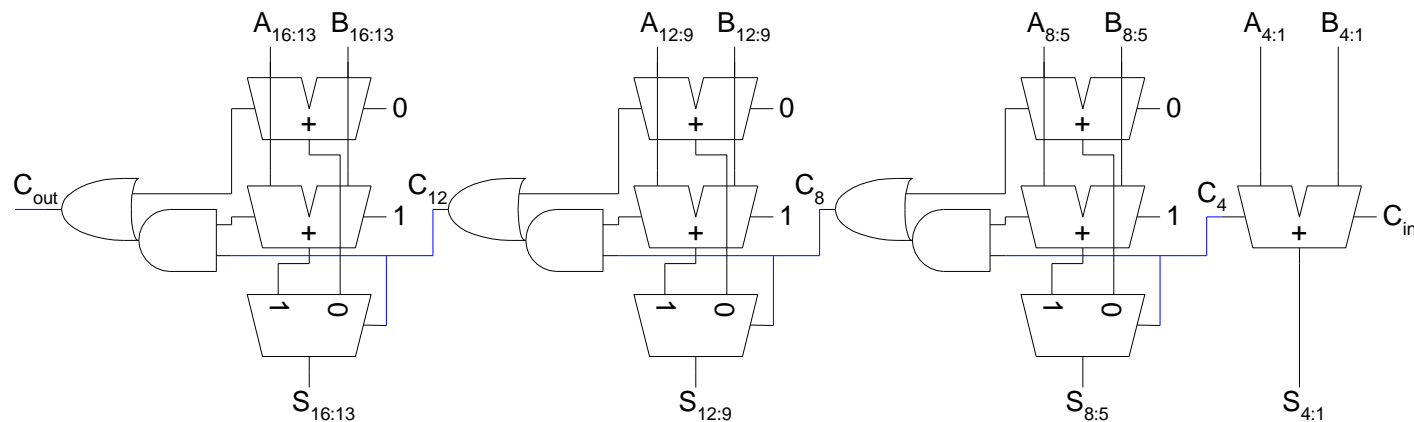
# Carry-Select Adder (CSA)

- For critical paths which are dependent on late input  $X$ ,
  - Precompute two possible outputs for  $X = 0, 1$
  - Select proper output when  $X$  arrives
- Carry-select adder precomputes  $n$ -bit sums for both possible carries into the  $n$ -bit group



$$t_{\text{select}} = t_{pg} + [n + (k - 2)]t_{AO} + t_{\text{mux}}$$

# Example Delay Optimization

- Consider designing an  $N$ -bit carry select adder (CSA) comprising of  $k$  groups of  $n$ -bits each ( $N=k \times n$ ). Write the expression for the worst-case delay from any input to any output in this adder. What are the optimum value for  $n$  and  $k$  which minimize the delay of the  $N$ -bit adder? What is the minimum delay of this adder?


$$Delay = t_{pg} + \left( \frac{N}{k} + k - 2 \right) t_{AO} + t_{mux}$$

$$\frac{\partial Delay}{\partial k} = -\frac{N}{k^2} + 1 = 0 \Rightarrow k = \sqrt{N}$$

$$Delay_{opt} = t_{pg} + 2(\sqrt{N} - 1)t_{AO} + t_{mux}$$
 
# Carry-Increment Adder (CIA)

- It uses a short ripple chain of black cells to compute the PG signals for bits within a group
- When the carry-out from the previous group becomes available, the final gray cells in each column determine the carry-out
- Higher-valency group PG cells can be used to speed up the ripple operation to produce the first group generate signals



$$t_{\text{increment}} = t_{pg} + [(n-1) + (k-1)]t_{AO} + t_{xor}$$


$$t_{\text{increment+CL}} = t_{pg} + t_{pg(n)} + (k-1)t_{AO} + t_{xor}$$

# Variable-Length CIA

- Use variable-length groups to utilize the fact that the more significant bits complete early

$$t_{\text{increment}} = t_{pg} + \sqrt{2N}t_{AO} + t_{xor}$$

 - Also do critical signal isolation by buffering along the noncritical signal paths







# (Prefix) Tree Adders

- If lookahead is good, lookahead across lookahead!
  - Recursive lookahead gives  $O(\log N)$  delay
- Many variations on tree adders (also known as logarithmic adders, multilevel-lookahead adders, and parallel-prefix adders)


# Brent-Kung

 


# Sklansky

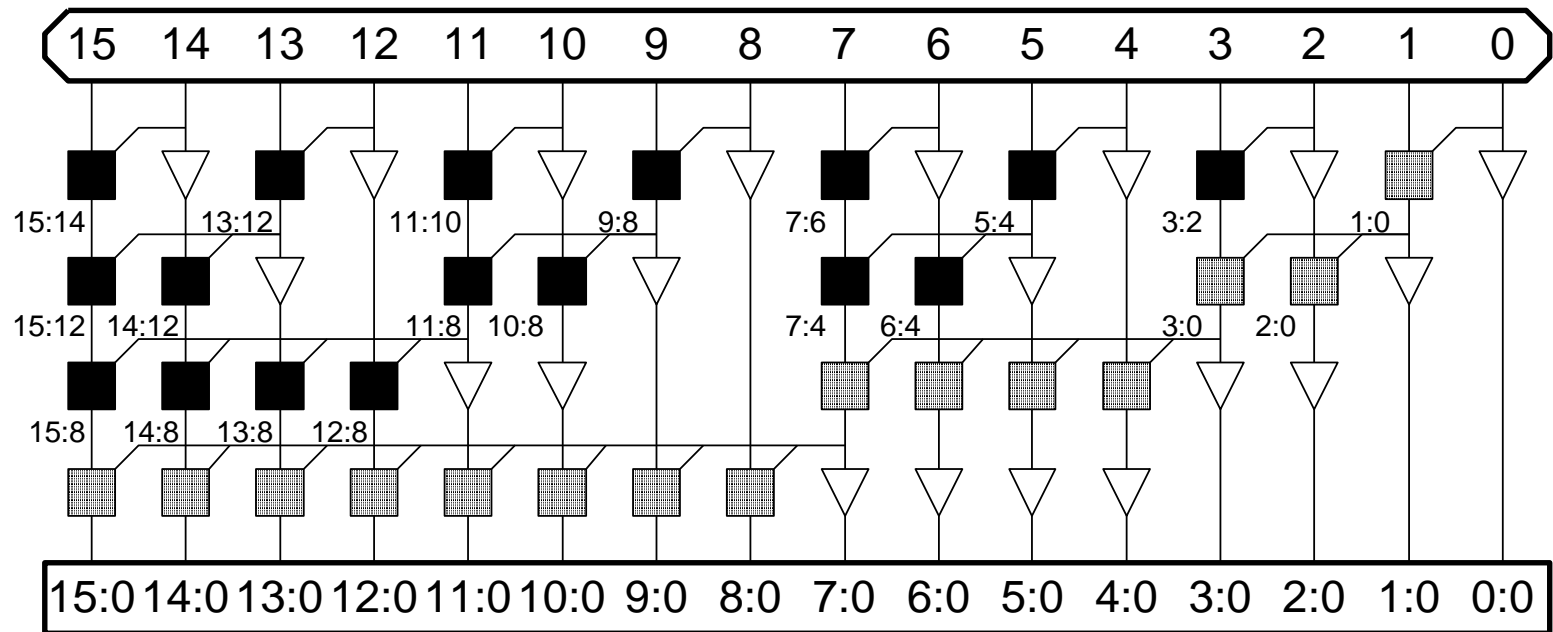


# Kogge-Stone

 


# Han-Carlson

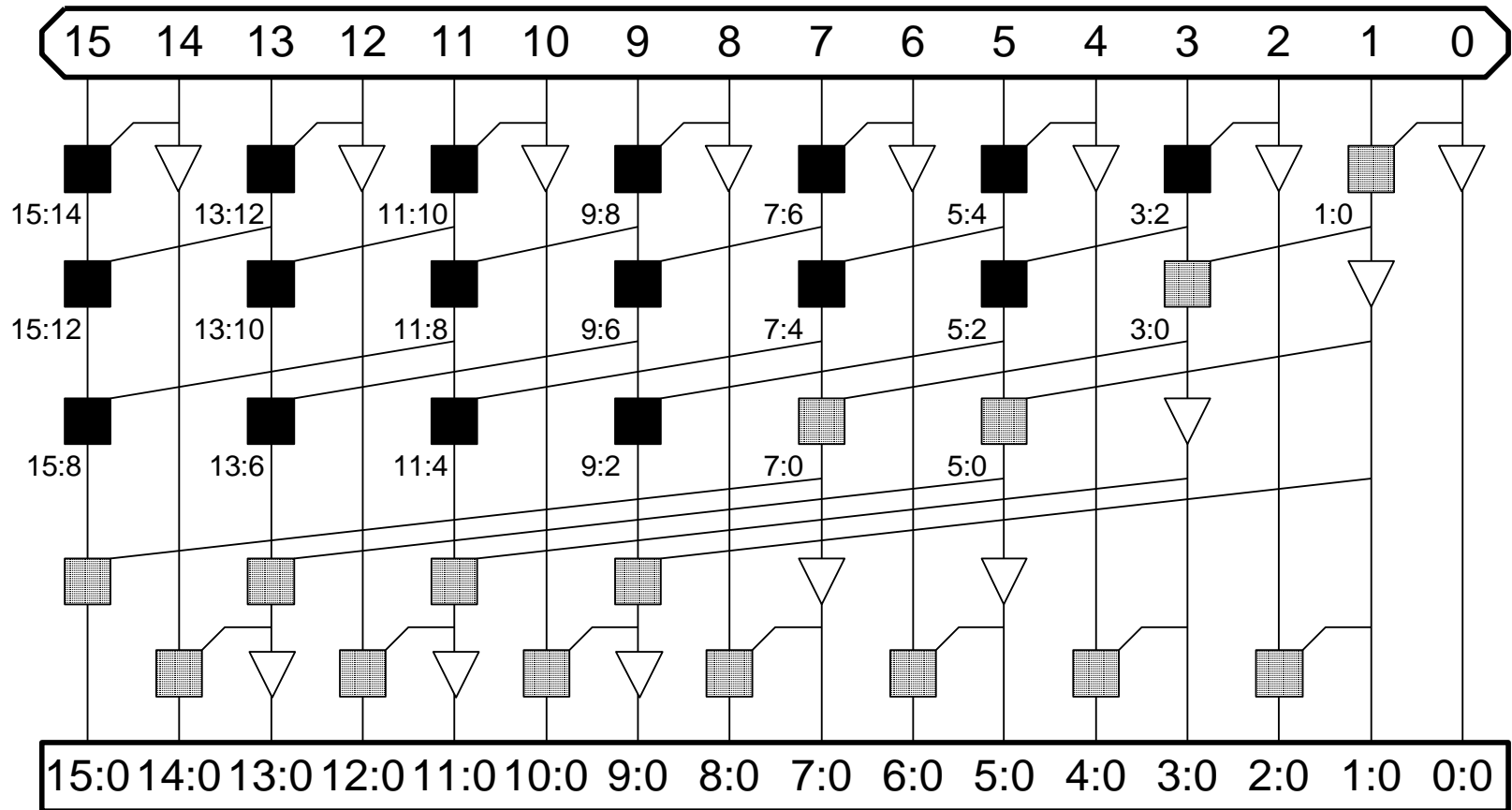

# Ladner-Fischer

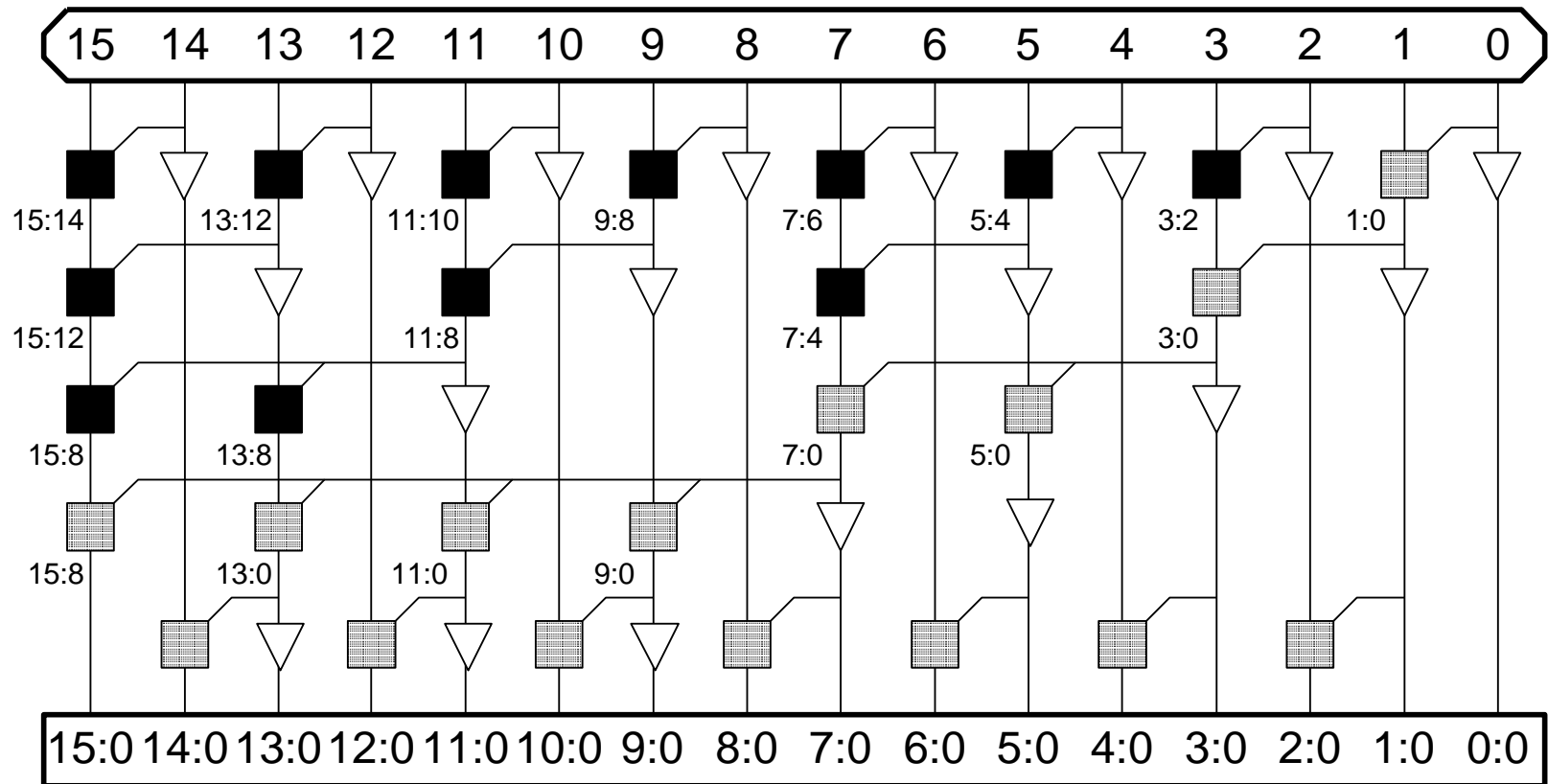


# Area vs. Delay Tradeoffs

 

Area vs. delay of synthesized adders
 
# Multi-input Adders


- Suppose we want to add  $k$   $N$ -bit words
  - Ex:  $0001 + 0111 + 1101 + 0010 = 10111$
- Straightforward solution:  $k-1$   $N$ -input CPAs
  - Large and slow





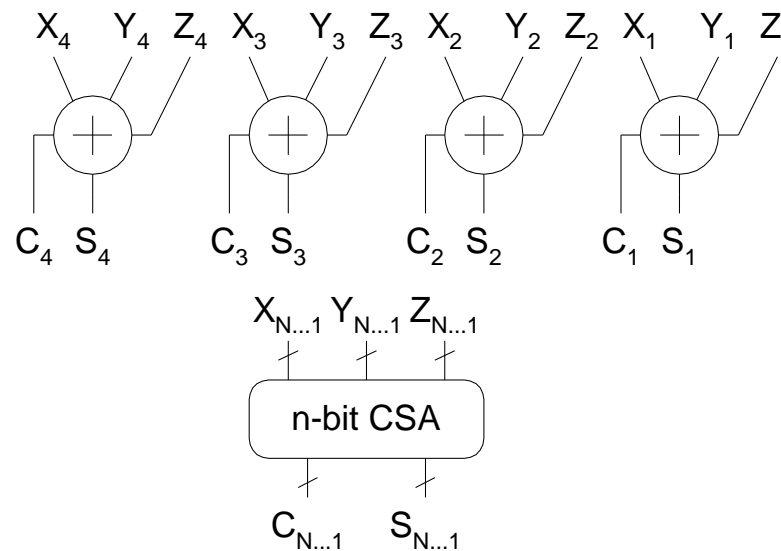
# Carry Save Addition

- A full adder sums 3 inputs and produces 2 outputs
  - Carry output has twice the *weight* of sum output
- N full adders in parallel are called *carry save adder*
  - Produce N sums and N carry outs


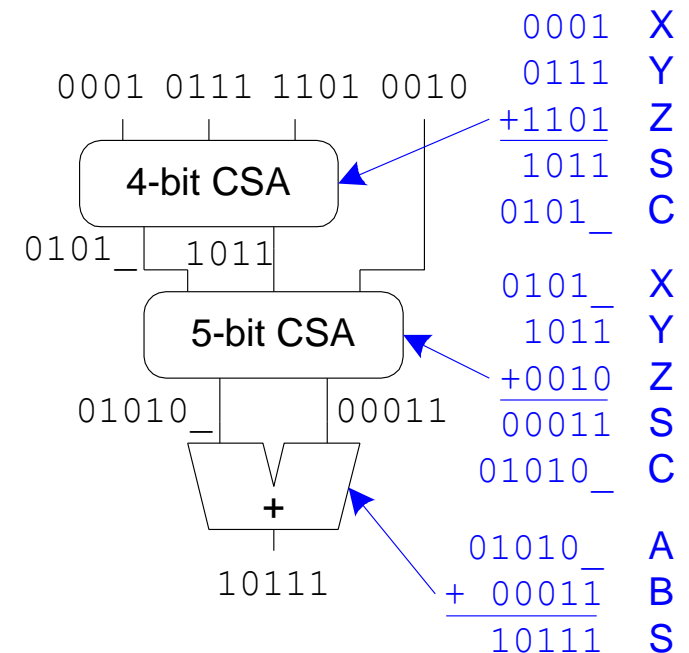
# CSA Application

- Use  $k - 2$  stages of CSAs
  - Keep result in carry-save redundant form
- Final CPA computes actual result



# Two's Complement

- A two's-complement system or two's-complement arithmetic is a system in which negative numbers are represented by the two's complement of the absolute value
- The two's complement of a binary number is the value obtained by subtracting the number from a large power of two (i.e., from  $2^N$  for an N-bit two's complement number)
- To negate a two's complement number, invert all the bits (which yields the one's complement), then add 1 to the result. Bit overflow is ignored, which is the normal case with zero

sign bit								
0	1	1	1	1	1	1	1	= 127
0	0	0	0	0	0	1	0	= 2
0	0	0	0	0	0	0	1	= 1
0	0	0	0	0	0	0	0	= 0
1	1	1	1	1	1	1	1	= -1
1	1	1	1	1	1	1	0	= -2
1	0	0	0	0	0	0	1	= -127
1	0	0	0	0	0	0	0	= -128

8-bit  
two's complement integers

$$11111011_2 = -128 + 64 + 32 + 16 + 8 + 0 + 2 + 1 = (-2^7 + 2^6 + \dots) = -5$$

# Sign Extension

- When turning a two's complement number with a certain number of bits into one with more bits (e.g., when copying from a 1 byte variable to a two byte variable), the sign bit must be repeated in all the extra bits

Decimal	4-bit two's complement	8-bit two's complement
5	0101	0000 0101
-3	1101	1111 1101

sign-bit repetition in  
4 and 8-bit integers

- Similarly, when a two's complement number is shifted to the right, the sign bit must be maintained. However when shifted to the left, a 0 is shifted in. These rules preserve the common semantics that left shifts multiply the number by two and right shifts divide the number by two

# Addition

- Adding two's complement numbers requires no special processing if the operands have opposite signs, that is, the sign of the result is determined automatically

$$\begin{array}{r} 1111\ 111\text{ (carry)} \\ 0000\ 1111\text{ (15)} \\ + 1111\ 1011\text{ (-5)} \\ \hline 0000\ 1010\text{ (10)} \end{array}$$

$$\begin{array}{r} 0111\text{ (carry)} \\ 0111\text{ (7)} \\ + 0011\text{ (3)} \\ \hline 1010\text{ (-6) invalid!} \end{array}$$

- This process depends upon restricting to N bits of precision; a carry to the (nonexistent) N+1<sup>st</sup> most significant bit is ignored, resulting in the arithmetically correct result
- If the last two carry bits (the ones on far left of the top row) are both 1's or both 0's, the result is valid; if the last two carry bits are "1 0" or "0 1", a sign overflow has occurred

# Subtraction


- Like addition, the advantage of using two's complement is the elimination of the need to examine signs of the operands to determine if addition or subtraction is needed

$$\begin{array}{r} 11110\ 000 \text{ (borrow)} \\ 0000\ 1111 \text{ (15)} \\ - 1111\ 1011 \text{ (-5)} \\ \hline 0001\ 0100 \text{ (20)} \end{array}$$

$$\begin{array}{r} 11100\ 000 \text{ (borrow)} \\ 0000\ 1111 \text{ (15)} \\ - 0010\ 0011 \text{ (35)} \\ \hline 1110\ 1100 \text{ (-20)} \end{array}$$

- Overflow is detected the same way as for addition, by examining the two leftmost (most significant) bits of the borrows; overflow has occurred when these two bits are different

# Subtraction Circuit

 

Subtractors

# Multiplication

- Example:**

1100	:	$12_{10}$	multiplicand
0101	:	$5_{10}$	multiplier
<hr/>			
1100			partial products
0000			
1100			
0000			
<hr/>			
00111100	:	$60_{10}$	product

- M x N-bit multiplication**
  - Produce N M-bit partial products
  - Sum these to produce M+N-bit product



# General Form

• **Multiplicand:**  $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$


• **Multiplier:**  $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

• **Product:** 
$$P = \left( \sum_{j=0}^{M-1} y_j 2^j \right) \left( \sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$



						$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$	multiplicand multiplier
						$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$	
						$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	partial products
					$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$		
				$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$			
			$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$				
		$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$					
	$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$						
$p_{11}$	$p_{10}$	$p_9$	$p_8$	$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$	product

# Dot Diagram


- Each dot represents a bit

 

# Four-Bit Multiplier

  

## Combinational Multiplier

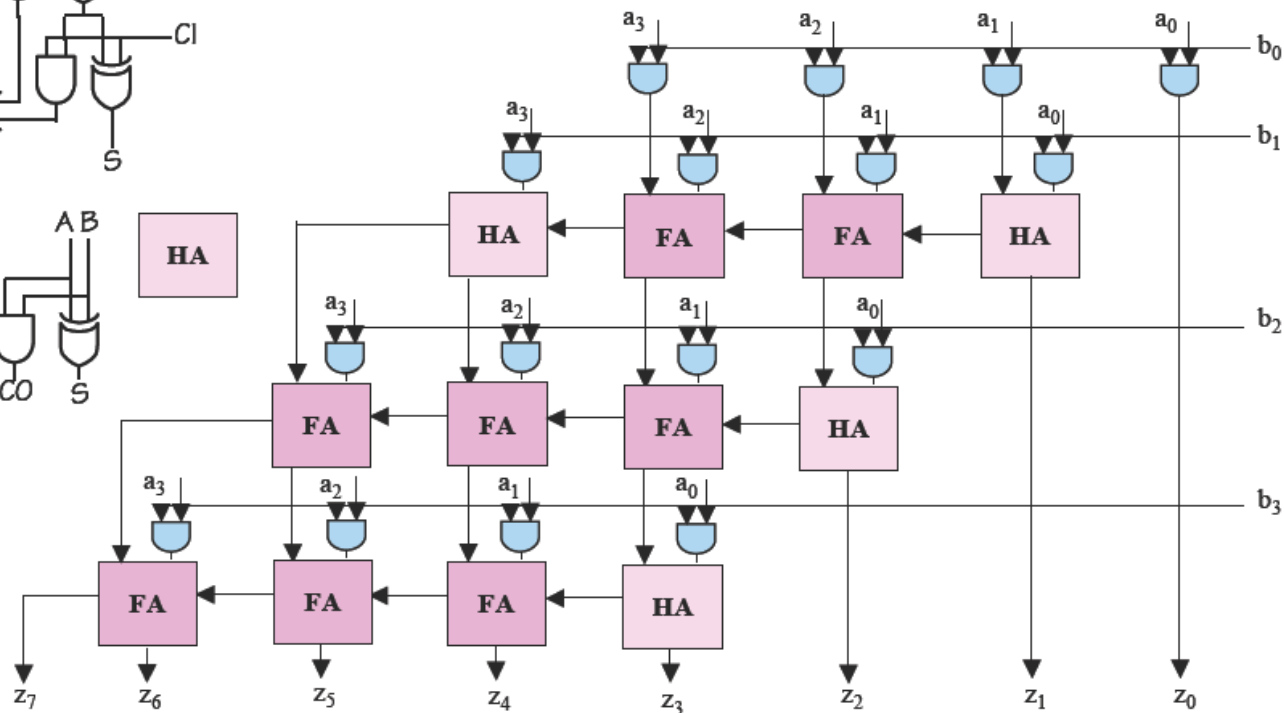

Latency =  $\Theta(N)$   
 Throughput =  $\Theta(1/N)$   
 Hardware =  $\Theta(N^2)$

# 2's Complement Array MUL

- Recall that the MSB of a 2's complement number has a negative weight

$$\begin{aligned} P &= \left( -y_{M-1}2^{M-1} + \sum_{j=0}^{M-2} y_j 2^j \right) \left( -x_{N-1}2^{N-1} + \sum_{i=0}^{N-2} x_i 2^i \right) \\ &= \sum_{i=0}^{N-2} \sum_{j=0}^{M-2} x_i y_j 2^{i+j} + x_{N-1} y_{M-1} 2^{M+N-2} - \left( \sum_{i=0}^{N-2} x_i y_{M-1} 2^{i+M-1} + \sum_{j=0}^{M-2} x_{N-1} y_j 2^{j+N-1} \right) \end{aligned}$$

# Baugh-Wooley MUL

[illegible]

### Partial products for 2's complement multiplier


# Simplified Partial Products

- Precompute the sums of the constant 1's and push some of the terms upward into extra columns


						$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
						$x_5$	$x_4$	$x_3$	$x_2$	$x_1$	$x_0$
					1	$\overline{x_5 y_0}$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$
				$\overline{x_5 y_1}$		$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$	
			$\overline{x_5 y_2}$	$x_2 y_4$		$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$		
		$\overline{x_5 y_3}$	$x_3 y_4$	$x_3 y_3$		$x_3 y_2$	$x_3 y_1$	$x_3 y_0$			
	$\overline{x_5 y_4}$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$		$x_4 y_1$	$x_4 y_0$				
1	$x_5 y_5$	$\overline{x_4 y_5}$	$\overline{x_3 y_5}$	$\overline{x_2 y_5}$	$\overline{x_1 y_5}$	$\overline{x_0 y_5}$					
$p_{11}$	$p_{10}$	$p_9$	$p_8$	$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$

Simplified partial products for 2's complement multiplier

# Four-Bit 2's Complement Multiplier

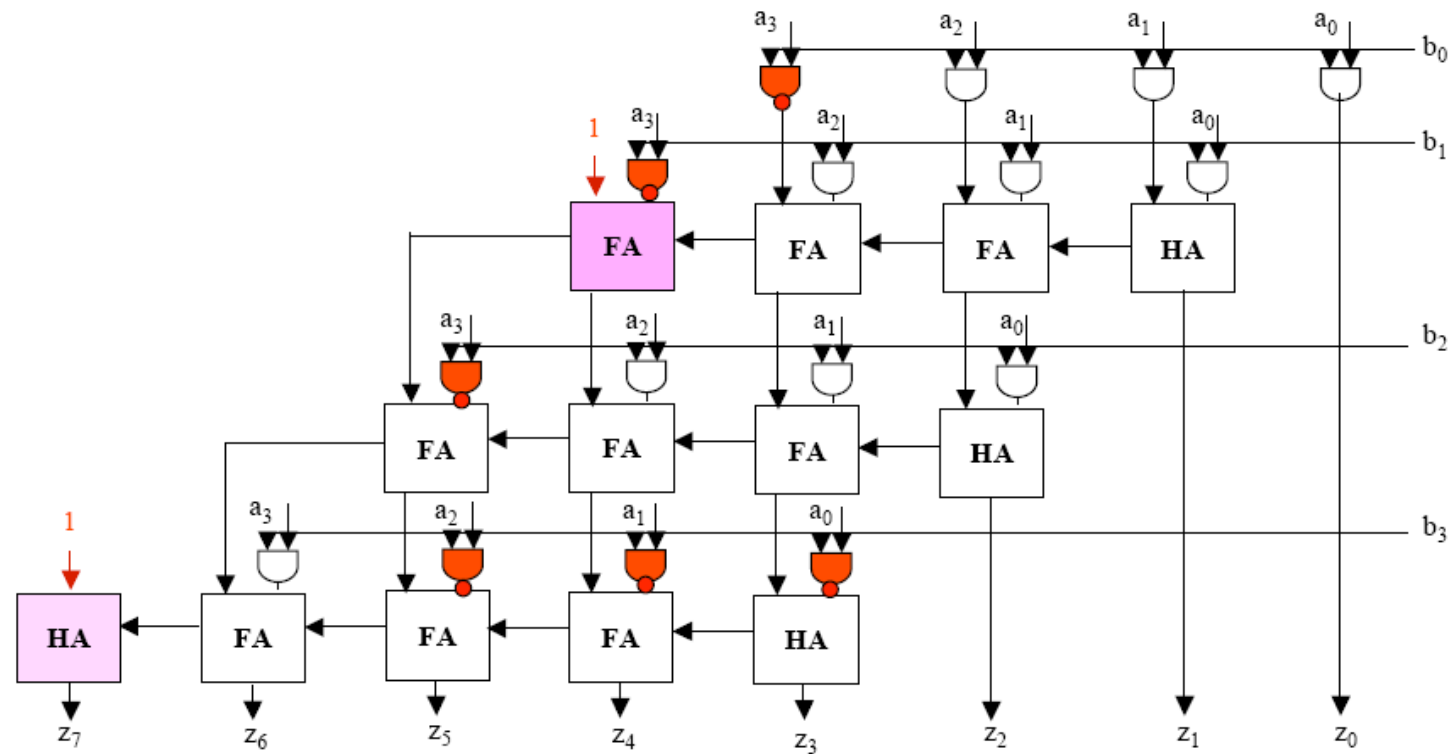


# Pipelining

 

- Maintains latency, but increases the throughput
  - Before pipelining:  $t_{clk} = t_F + t_R + t_X + t_M + t_W$
  - After pipelining:  $t_{clk} = \max(t_F, t_R, t_X, t_M, t_W) + t_{ck2q} + t_{setup}$



# Increase Throughput with Pipelining

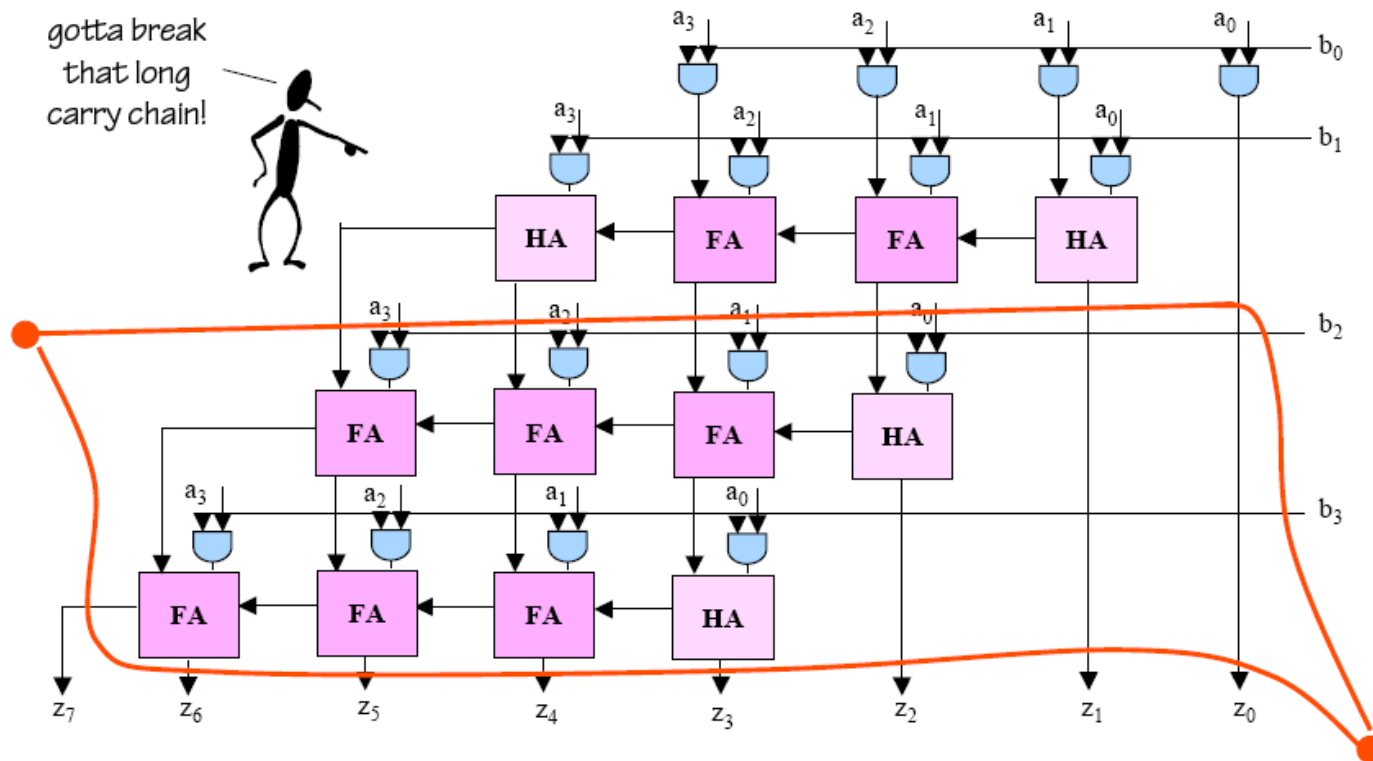

Before pipelining: Throughput =  $\sim 1/(2N) = \Theta(1/N)$

After pipelining: Throughput =  $\sim 1/N = \Theta(1/N)$