

University of Southern California

Viterbi School of Engineering

EE577A

VLSI System Design

Static Timing Analysis

References: syllabus textbook, online resources


Shahin Nazarian

Spring 2013

Background

- Objective
- Delay dependencies
- Timing models

Steps in Static Timing Analysis

 


- Circuit is broken down into sets of timing paths
- Delay of each path is calculated
- Path delays are checked to see if timing constraints have been met

Delay Models

- Delay Model Classification
 - Linear
 - Nonlinear

K-Factor Gate Delay

 - K-factor equation
 - Delay $t_d = k(t_{r/f}, C_{total})$
 - Output transition time $t'_{r/f} = k'(t_{r/f}, C_{total})$
- Example of K-factor form:
 - Delay = $a \cdot t + b \cdot C_{total} + c \cdot t \cdot C_{total} + d$
 - Obtained from SPICE simulation



NLDM Lookup Tables

```
cell_fall(delay_template_3x4) {  
  index_1 ("0.1, 0.4, 0.9"); /* Input transition */  
  index_2 ("0.11, 0.25, 1.31, 2.55"); /* Output capacitance */  
  values ( /* 0.11 0.25 1.31 2.55 */ \  
    /* 0.1 */ "0.0617, 0.1537, 0.5280, 0.9338", \  
    /* 0.4 */ "0.0918, 0.2027, 0.5676, 0.9547", \  
    /* 0.9 */ "0.1034, 0.2273, 0.6452, 1.0984");  
}
```

NLDM Lookup Tables (Cont.)

- Interpolation

$$T_{IP} = x_{20} * y_{20} * T_{11} + x_{20} * y_{01} * T_{12} + x_{01} * y_{20} * T_{21} + x_{01} * y_{01} * T_{22}$$

- where

$$x_{01} = (x_0 - x_1) / (x_2 - x_1)$$

$$x_{20} = (x_2 - x_0) / (x_2 - x_1)$$



$$y_{01} = (y_0 - y_1) / (y_2 - y_1)$$

$$y_{20} = (y_2 - y_0) / (y_2 - y_1)$$

NLDM Lookup Tables (Cont.)

- Slew derating
 - Slew to represent the linear portion
 - Current vs old slew measurement
 - Example: Derating factor of 0.5 for (10%, 90%) measurement to (30%, 70%)

Effective Capacitance

  

$$C_{eff} = C_1 + kC_2 \quad 0 < k < 1$$



- Because of the shielding effect of the interconnect resistance, the driver will only “see” a portion of the far-end capacitance C_2

$$R_\pi \longrightarrow 0 \quad \text{---} \quad k = 1$$

$$R_\pi \longrightarrow \infty \quad \text{---} \quad k = 0$$

Timing Models - Combinational Cells

  - Timing arcs: represent the propagation delays through the cell
 - Positive vs negative unate



Timing Models - Sequential Cells



- Synchronous inputs
- Synchronous outputs



Sequential Elements


- Synchronous inputs
- Synchronous outputs

Sequential Cells - Latch

  


Sequential Cells - Latch (Cont.)

(a)

 


(b)

 


Sequential Cells - Metastability

 
- Being in a metastable state, the flip-flop may be unable to stabilize and this may finally result in a faulty output





Sequential Cells - D Flip-Flop

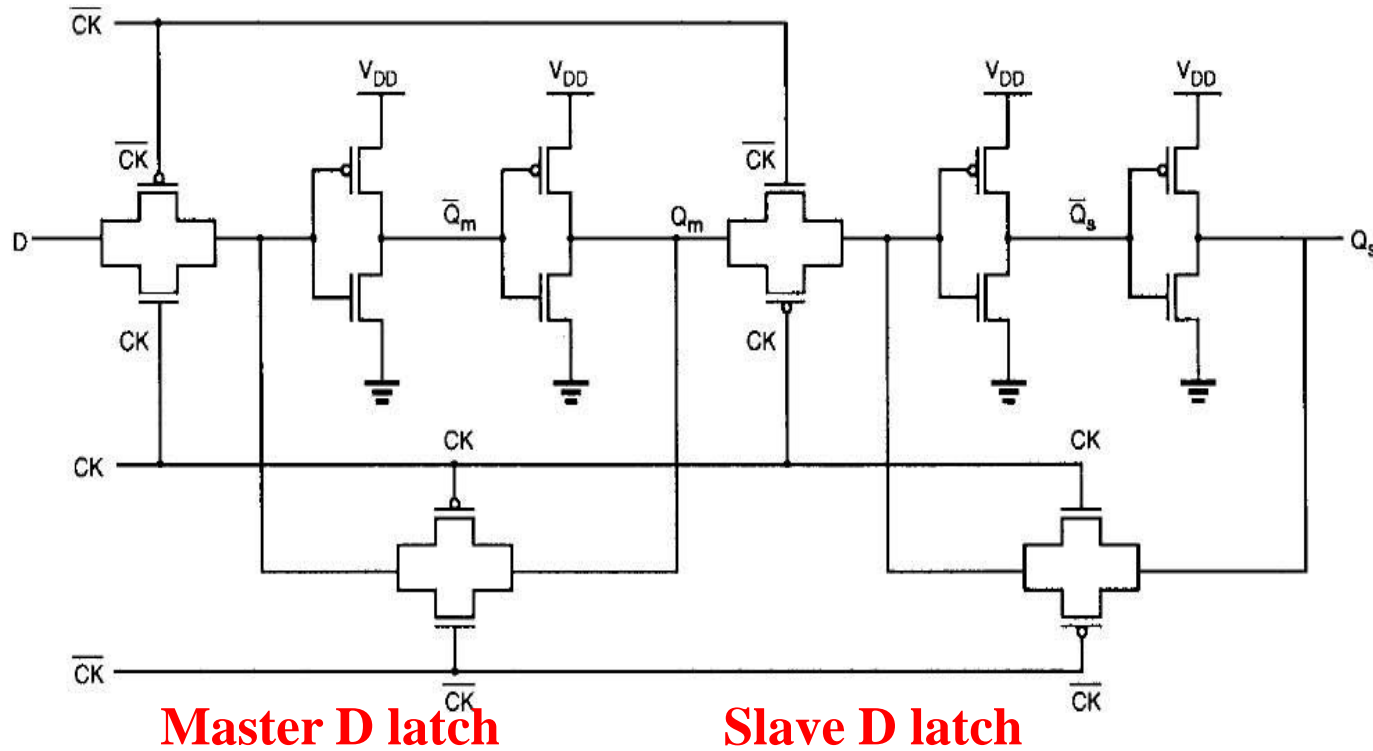


Sequential Cells - D Flip-Flop

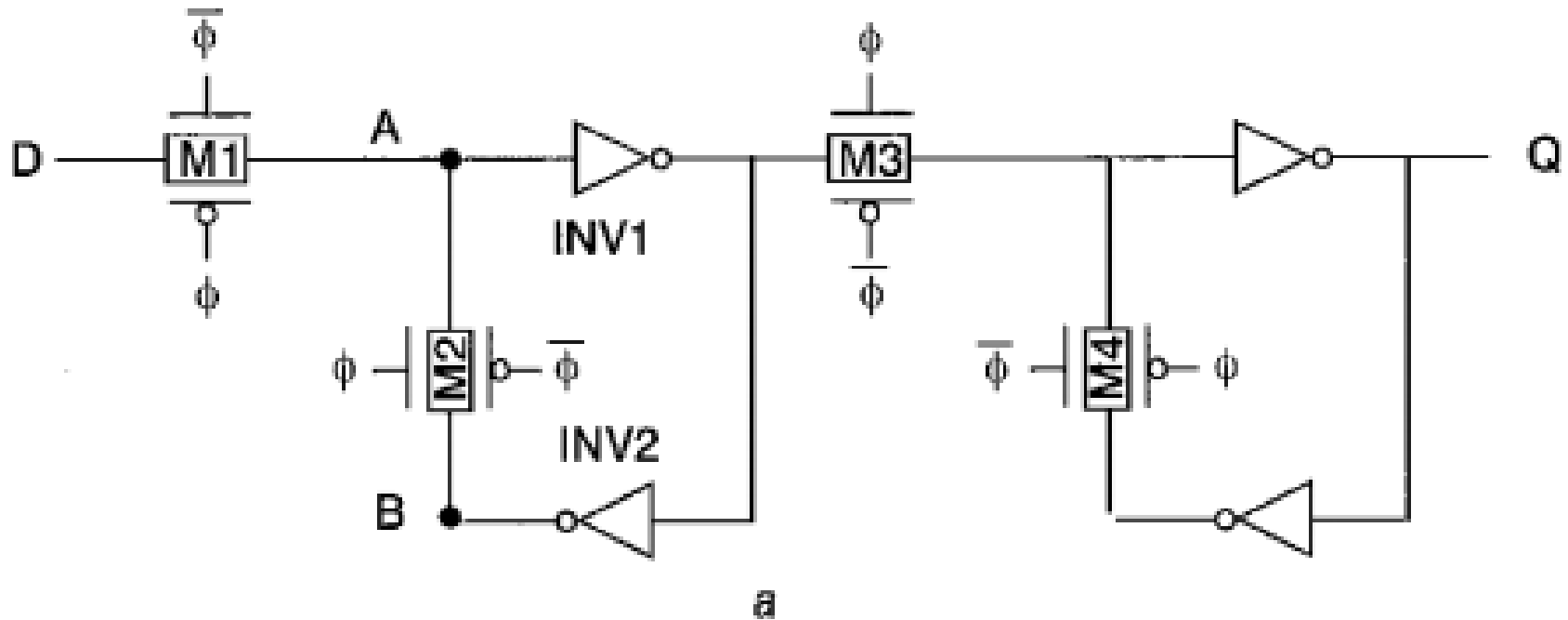

Clock-to-Q Delay and Timing Constraints

  

Setup and Hold Checks

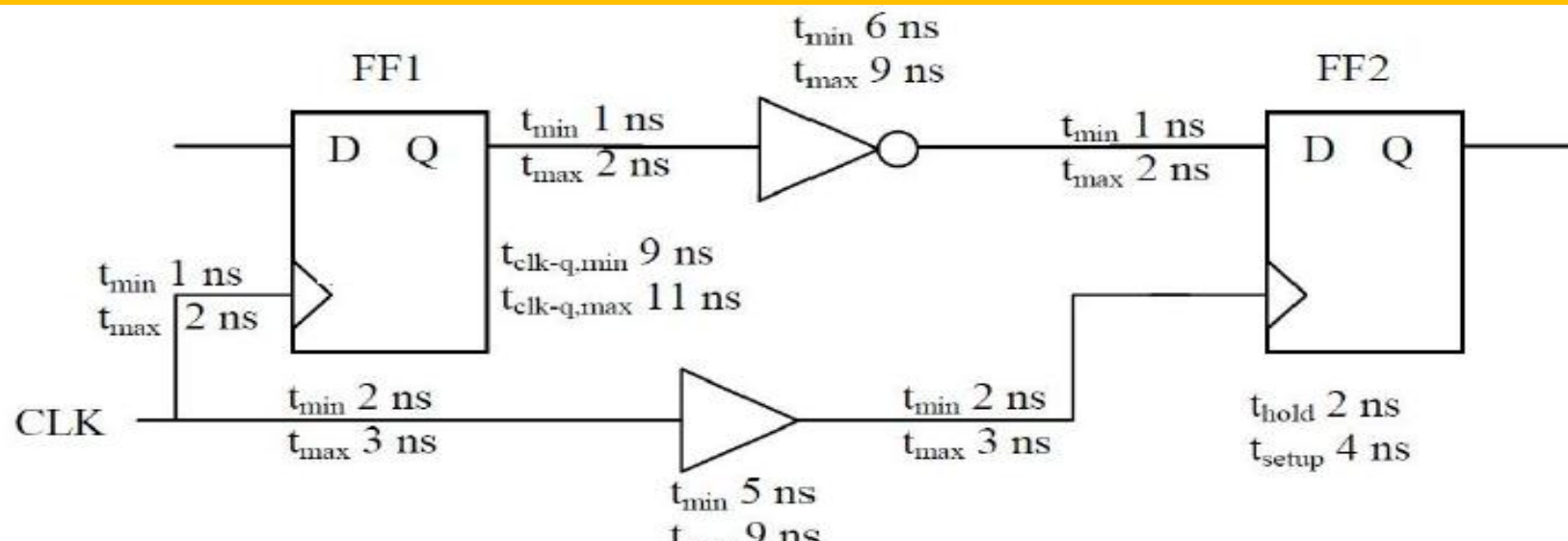

For SETUP :


Delay in Data path = $\max(\text{wire delay to the clock input of FF1}) + \max(\text{Clk-to-Q delay of FF1}) + \max(\text{cell delay of inverter}) + \max(2 \text{ wire delay - "Q of FF1-to-inverter" and "inverter-to-D of FF2"}) = T_d = 2 + 11 + 9 + (2 + 2) = 26 \text{ ns}$

Clock path Delay = (Clock period) + $\min(\text{wire delay from CLK to Buffer input}) + \min(\text{cell delay of Buffer}) + \min(\text{wire delay from Buffer output to FF2/CLK pin}) - (\text{Setup time of FF2})$
 $= T_{clk} = 15 + 2 + 5 + 2 - 4 = 20 \text{ ns}$

Setup Slack = $T_{clk} - T_d = 20 \text{ ns} - 26 \text{ ns} = -6 \text{ ns}$.

Since Setup Slack is negative \rightarrow Setup violation.

Setup and Hold Checks (Cont.)

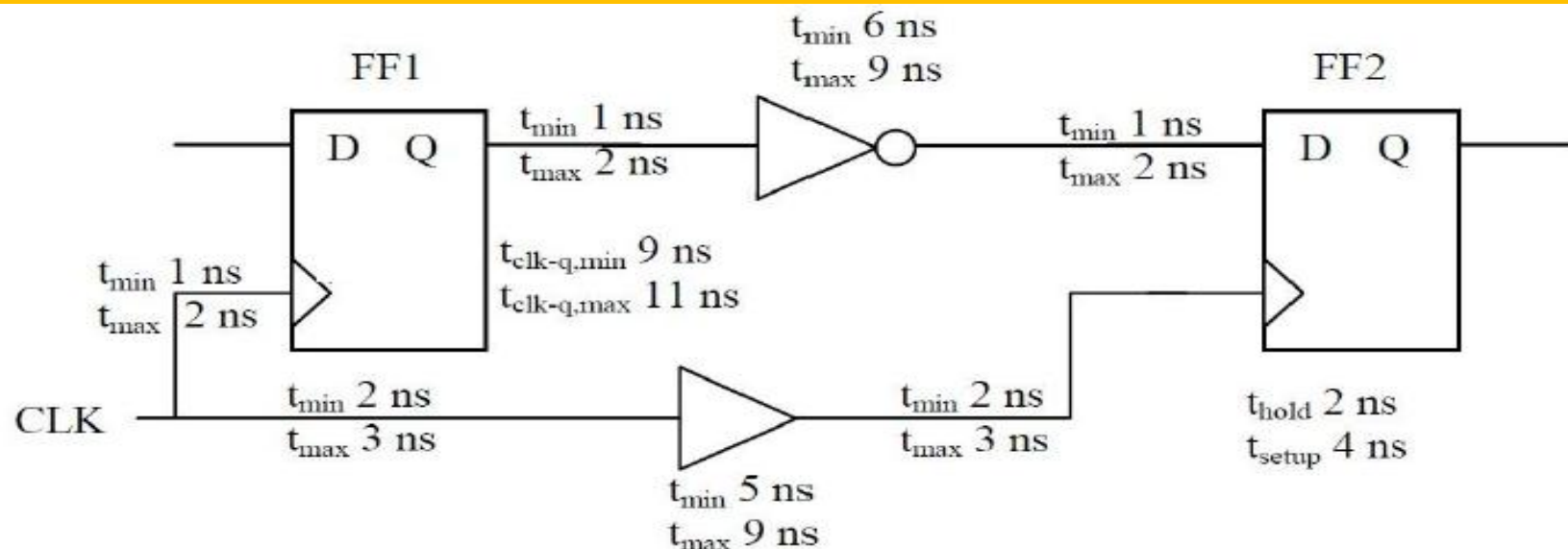

For HOLD :

Delay in Data path = $\min(\text{wire delay to the clock input of FF1}) + \min(\text{Clk-to-Q delay of FF1}) + \min(\text{cell delay of inverter}) + \min(2 \text{ wire delay - "Q of FF1-to-inverter" and "inverter-to-D of FF2"}) = T_d = 1 + 9 + 6 + (1 + 1) = 18 \text{ ns}$


Clock path Delay = $\max(\text{wire delay from CLK to Buffer input}) + \max(\text{cell delay of Buffer}) + \max(\text{wire delay from Buffer output to FF2/CLK pin}) + (\text{hold time of FF2}) = T_{clk} = 3 + 9 + 3 + 2 = 17 \text{ ns}$

Hold Slack = $T_d - T_{clk} = 18 \text{ ns} - 17 \text{ ns} = 1 \text{ ns}$

Since Hold Slack is positive-> No hold Violation.

Output required time

 - Output required time
 - Specifies the data required time on output ports




Slack and Critical path

- Slack is the difference between the required (constraint) time and the arrival time (inputs and delays)
 - Negative slack indicates that constraints have not been met, while positive slack indicates that constraints have been met
 - Slack analysis is used to identify timing critical paths in a design by the static timing analysis tool
- Critical path
 - Any logical path in the design that violates the timing constraints
 - Path with a negative slack

Interconnect (Net) Delay

 - “Net Delay” refers to the total time needed to charge or discharge all of the parasitics of a given net
- Total net parasitics are affected by
 - Net length
 - Net fanout
- Net delay and parasitics are typically
 - Back-Annotated (Post-Layout) from data obtained from
 - An extraction tool
 - Estimated (Pre-Layout)




Optional: Transmission Line Equations

- Drop across R and L is :

$$\frac{\partial V}{\partial x} = RI + L \frac{\partial I}{\partial t}$$

- Current through C and G is :
 
$$\frac{\partial I}{\partial x} = GV + C \frac{\partial V}{\partial t}$$



**Infinitesimal Model of
a Transmission Line**


- The resulting equation is as follows:

$$\frac{\partial^2 V}{\partial x^2} = RGV + (RC + LG) \frac{\partial V}{\partial t} + LC \frac{\partial^2 V}{\partial t^2}$$


Mutual Inductance and Capacitance

- Crosstalk is the coupling of energy from one line to another via:
 - Mutual capacitance (electric field)
 - Mutual inductance (magnetic field)

Mutual Capacitance, C_m

 

Mutual Inductance, L_m

 

Mutual (Cont.)


- The circuit element that represents this transfer of energy are the following familiar equations

$$V_{Lm} = L_m \frac{dI}{dt} \qquad I_{Cm} = C_m \frac{dV}{dt}$$

- The mutual inductance will induce current on the victim line opposite of the driving current (Lenz's Law)
- The mutual capacitance will pass current through the coupling (mutual) capacitance that flows in both directions on the victim line


Crosstalk Induced Noise

 - The near and far end victim line currents sum to produce the near and the far end crosstalk noise



$$I_{near} = I_{Cm} + I_{Lm} \quad I_{far} = I_{Cm} - I_{Lm}$$

Crosstalk Induced Noise (Cont.)

 


$$I_1 = C_{1g} \frac{dV_1}{dt} + C_m \frac{d(V_1 - V_2)}{dt} = (C_{1g} + C_m) \frac{dV_1}{dt} - C_m \frac{dV_2}{dt}$$

$$I_2 = C_{2g} \frac{dV_2}{dt} + C_m \frac{d(V_2 - V_1)}{dt} = (C_{2g} + C_m) \frac{dV_2}{dt} - C_m \frac{dV_1}{dt}$$

False Paths

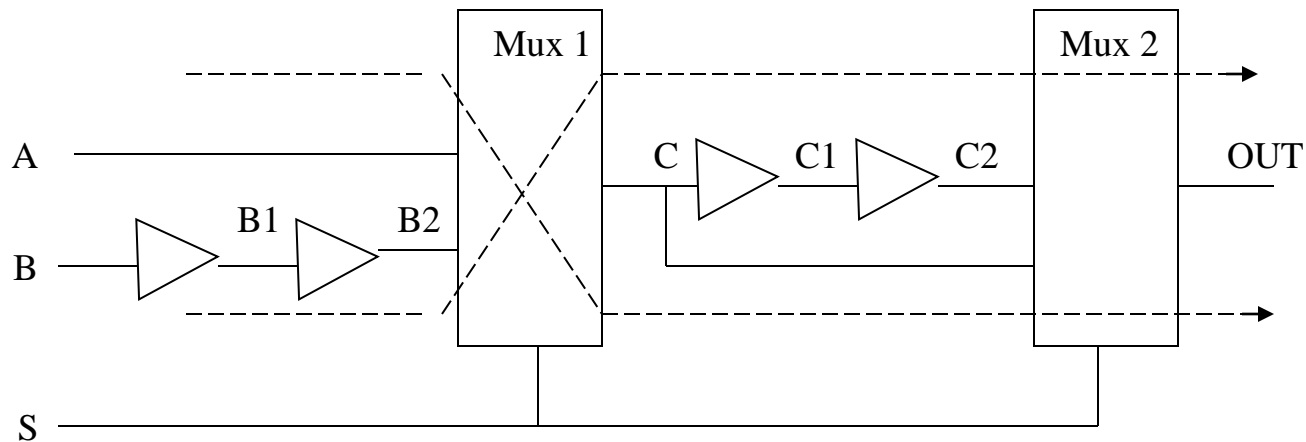- Paths that physically exist in a design but are not logic/functional paths
- These paths never get sensitized under any input conditions



Multi-cycle paths

- Data Paths that require more than one clock period for execution

