

University of Southern California

Viterbi School of Engineering

EE577A
VLSI System Design

Introduction


**References: Professor Massoud Pedram's lecture slides,
books listed in the syllabus, and online resources**

Shahin Nazarian

Spring 2013

EE577A Objectives

Two-Terminal MOS Structure

 


Under thermal equilibrium (Mass Action Law)

$$np = n_i^2 \quad (n_i \approx 1.45 \times 10^{10} \text{ cm}^{-3})$$


If substrate is uniformly doped @ N_A (Typically 10^{14} to 10^{16})

$$p_{p0} = N_A \rightarrow n_{p0} \approx \frac{n_i^2}{N_A}$$


Structure of MOS Transistor

 

 - The inverted surface layer is essential for current conduction. The two n+ regions are added as the current conducting terminals
- Conventionally all terminal voltages are defined wrt V_S




Threshold Voltage

 

- Channel behavior is exactly as that of a metal-gate-oxide: increase V_G and surface is inverted as soon as surface potential reaches a critical threshold voltage V_{T0}
- Note that increasing V_{GS} beyond V_{T0} will not increase the depletion region depth
- V_{DS} would then allow current flow


nMOS - Accumulation

n-MOS transistor
Accumulation Mode

 


nMOS - Depletion


n-MOS transistor
Depletion Mode

 


nMOS - Inversion

 


nMOS Linear and Saturation Operations

 

Operating in the linear region

 

Operating at the edge of saturation

 


Operating beyond saturation



CMOS Processing Technology Steps

Useful link:

<http://semiconductorglossary.com/>

 

 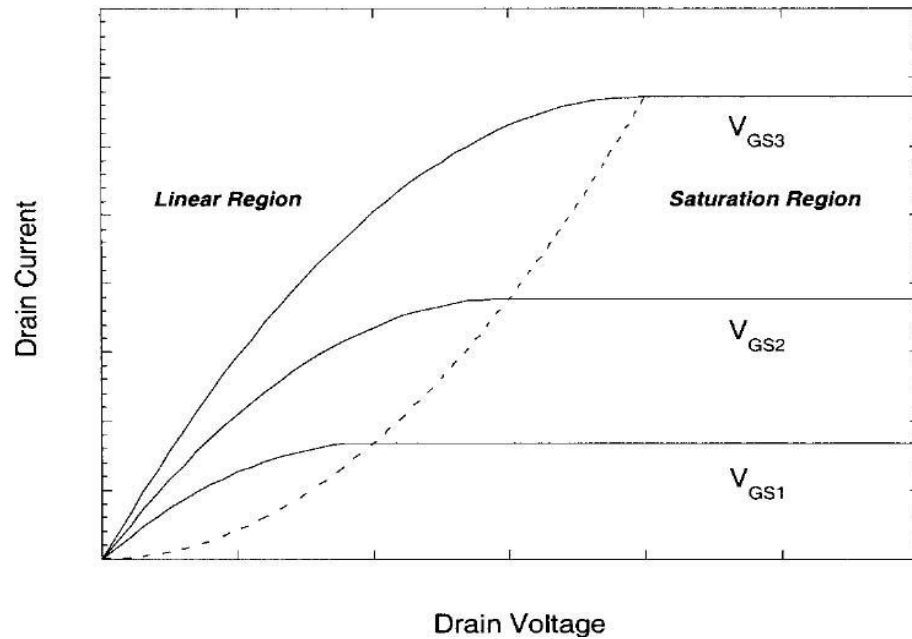NMOS I_D - V_{DS} and I_D - V_{GS} Curves



$$I_D(\text{lin}) = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left(2(V_{GS} - V_{T0})V_{DS} - V_{DS}^2 \right)$$

$$I_D(\text{sat}) = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{T0})^2$$


Channel Length Modulation

- The channel is pinched off under saturation condition; The pinch-off point moves from the drain end towards source as V_{DS} increases:

$$I_{Dsat} \propto \frac{1}{L - \Delta L} \cong \frac{1}{L} \left(1 + \frac{\Delta L}{L} \right) \quad \text{where} \quad \frac{\Delta L}{L} = \lambda V_{DS}$$

- We can then write the saturation current as:
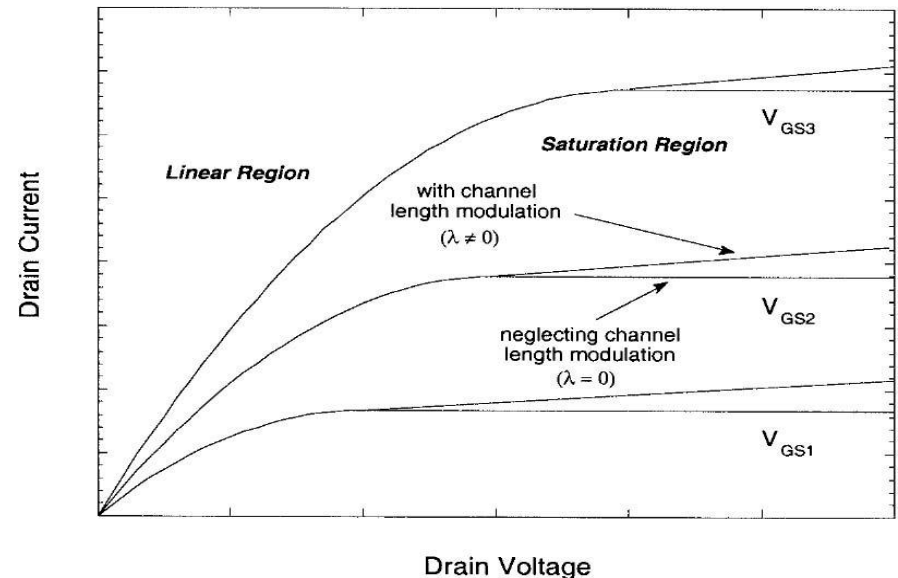
$$I_D(sat) = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{T0})^2 (1 + \lambda V_{DS})$$





Substrate Bias Effect

- Applying a substrate voltage changes the threshold voltage

$$V_T(V_{SB}) = V_{T0} + \gamma \left(\sqrt{|2\phi_F| + V_{SB}} - \sqrt{|2\phi_F|} \right)$$

- We can simply replace the threshold voltage terms in linear-mode and saturation-mode current equations with $V_T(V_{SB})$
  
$$I_D(\text{lin}) = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left(2(V_{GS} - V_T(V_{SB}))V_{DS} - V_{DS}^2 \right)$$
$$I_D(\text{sat}) = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T(V_{SB}))^2 (1 + \lambda V_{DS})$$



MOSFET Current-Voltage Equations (a.k.a. Shichman-Hodges Equations)

- **nMOS transistor, with**

$$k_n = k'_n \frac{W}{L} = \mu_n C_{ox} \frac{W}{L}$$

$$I_D(cutoff) = 0 \quad V_{GS} < V_T$$

$$I_D(lin) = \frac{k_n}{2} \left(2(V_{GS} - V_T(V_{SB}))V_{DS} - V_{DS}^2 \right) \quad V_{GS} \geq V_T, V_{DS} < V_{GS} - V_T$$

$$I_D(sat) = \frac{k_n}{2} (V_{GS} - V_T(V_{SB}))^2 (1 + \lambda V_{DS}) \quad V_{GS} \geq V_T, V_{DS} \geq V_{GS} - V_T$$

- **pMOS transistor, with**

$$k_p = k'_p \frac{W}{L} = \mu_p C_{ox} \frac{W}{L}$$

$$I_D(cutoff) = 0 \quad V_{GS} > V_T$$

$$I_D(lin) = \frac{k_p}{2} \left(2(V_{GS} - V_T(V_{SB}))V_{DS} - V_{DS}^2 \right) \quad V_{GS} \leq V_T, V_{DS} > V_{GS} - V_T$$

$$I_D(sat) = \frac{k_p}{2} (V_{GS} - V_T(V_{SB}))^2 (1 + \lambda V_{DS}) \quad V_{GS} \leq V_T, V_{DS} \leq V_{GS} - V_T$$

Example

- For an n-channel MOS transistor with $\mu_n=600$ $\text{cm}^2/\text{V.s}$, $C_{ox}=7 \times 10^{-8}$ F/cm^2 , $W=20$ μm , $L=2$ μm and $V_{T0}=1.0$ V , plot the relationship between I_D and the terminal voltages


$$k = 600 \text{ cm}^2 / \text{V.s} \times 7 \times 10^{-8} \text{ F} / \text{cm}^2 \times \frac{20 \mu\text{m}}{2 \mu\text{m}} = 0.42 \text{ mA/V}^2$$

For Linear operation:

$$V_{GS} \geq V_{T0}$$


$$V_{GD} = V_{GS} - V_{DS} \geq V_{T0} \Rightarrow V_{DS} \leq V_{GS} - V_{T0}$$
 
$$I_D = 0.21 \text{ mA/V}^2 \left[2(V_{GS} - 1)V_{DS} - V_{DS}^2 \right]$$



NMOS Transistors in Series/Parallel Connection


 
- Transistors can be thought as a switch controlled by its gate signal
- NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1

PMOS Transistors in Series/Parallel Connection

  
- PMOS switch closes when switch control input is low



PMOS Transistors pass a “strong” 1 but a “weak” 0


Threshold Drops

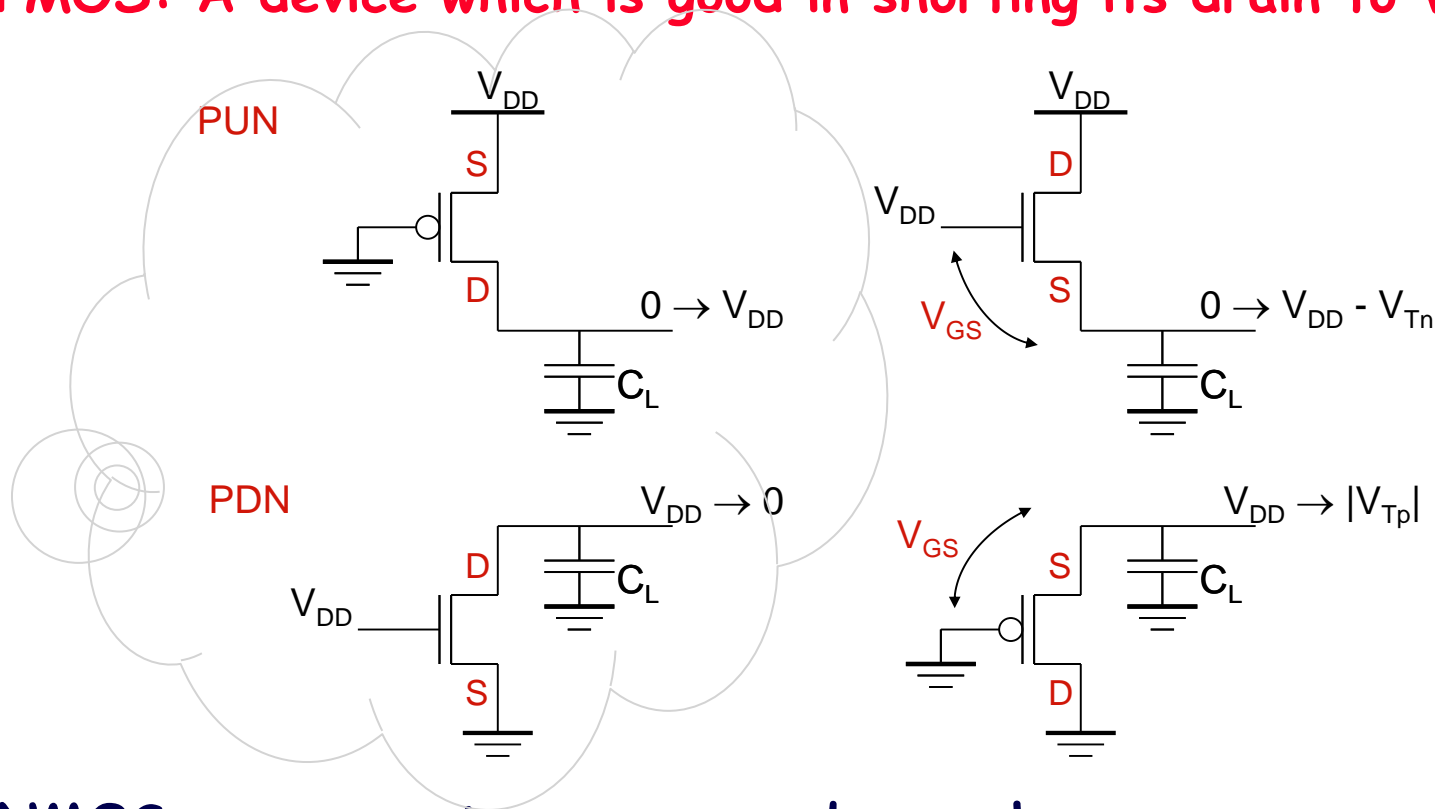- **NMOS:** A device which is good in shorting its drain to the ground
- **PMOS:** A device which is good in shorting its drain to V_{DD}



- **NMOS** passes a strong zero and a weak one
- **PMOS** passes a strong one and a weak zero
- **Note:** NMOS gate = 0, PMOS gate = 1 are in high Impedance


CMOS NOR2 Gate

 


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

Complex (Static) CMOS Gates

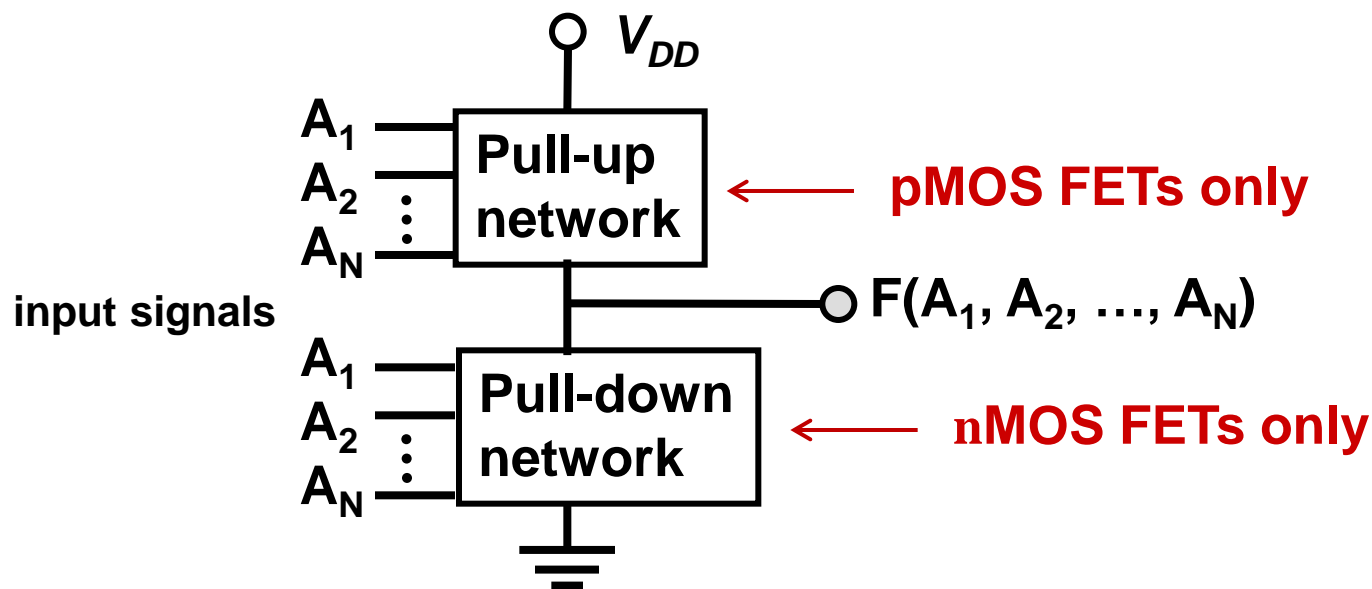- In CMOS logic gates, nMOS FETs are used to connect the output to GND, whereas pMOS FETs are used to connect the output to V_{DD}
 - An nMOS FET functions as a pull-down device when it is turned on (gate voltage = V_{DD})
 - A pMOS FET functions as a pull-up device when it is turned on (gate voltage = GND)




Reduction of Complex Gates to Inverters

 

- Note that reduction for worst case t_{pHL} is:

$$\left(\frac{W}{L}\right)_{\text{worstcasedelay},Z} = \text{MIN} \left[\left(\frac{W}{L}\right)_D, \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_B}}, \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_C}} \right]$$


Sizing - Complex CMOS Gates

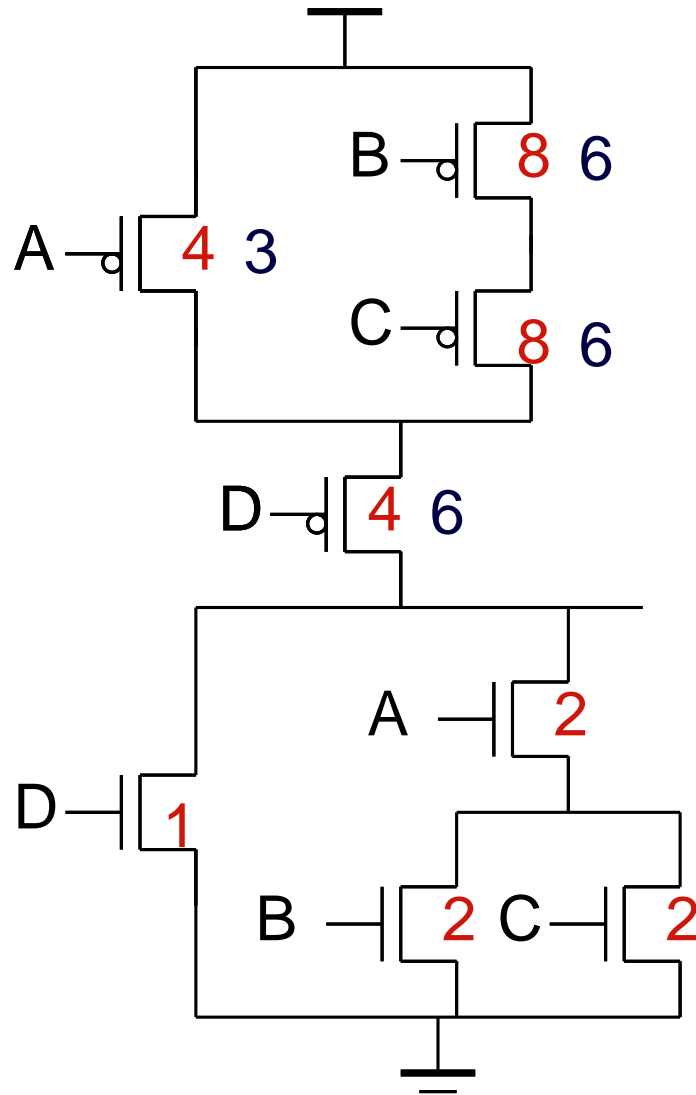

$$\text{OUT} = \overline{D + A \cdot (B + C)}$$


Layout Design - Stick Diagram

 - Construction of the dual pull-up graph from the pull-down graph



Stick Diagram (Cont.)


- The number of diffusion breaks can be minimized by changing the ordering of the polysilicon columns
- A simple method for finding the optimum gate ordering is the Euler-path approach
 - Find a common Euler path for both pull-down and pull-up graphs
 - The polysilicon columns can be arranged according to the sequence (in Euler-path)
- Diffusion will be unbroken if identically labeled Euler paths can be found for the p and n trees

 

nMOS network

Common Euler Path


E - D - A - B - C

 


pMOS network

Layout of Complex Gates (Cont.)

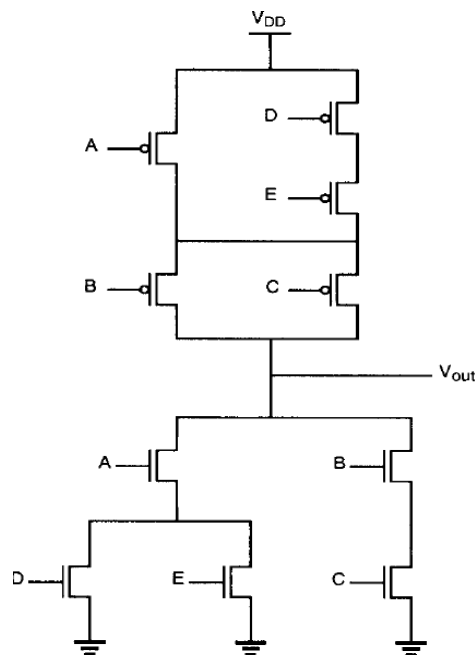- Optimize stick-diagram layout of the complex CMOS logic gate



 
Optimized stick-diagram layout of the complex CMOS logic gate



- The advantages of this new layout are more compact layout area, simple routing of signals, and consequently, lower parasitic capacitance

CMOS Transmission Gates (Pass Gates)


 
- The CMOS **transmission gate (TG)** consists of one NMOS and one PMOS transistor, connected in parallel
- The CMOS TG operates as a bidirectional switch between nodes A and B, which is controlled by signal C



Four different representations of the CMOS transmission gate


Model of a CMOS TG

  - A CMOS pass gate which is turned on by a logic-high control signal can be replaced by its **simple equivalent resistance** for dynamic analysis



Pass Gate Resistance Calculation

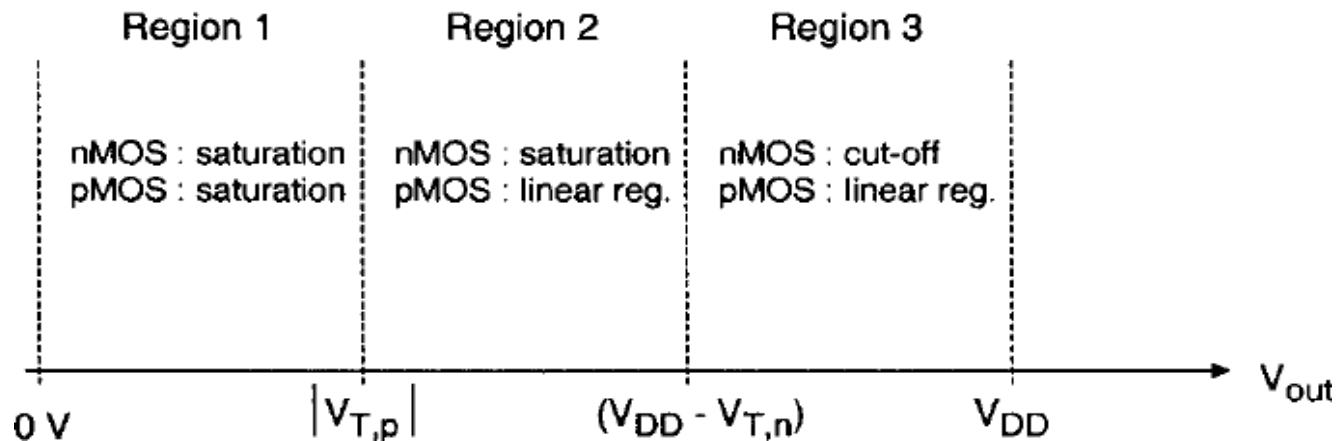- Unlike the nMOS transistor, the pMOS remains ON regardless of V_{out}
- If nMOS is ON, it would be in saturation region
- We can identify three operating regions for the CMOS transmission gate, depending on the output voltage level



- The total current flowing through the transmission gate is the sum of the nMOS drain and the pMOS drain current:

$$I_D = I_{DS,n} + I_{SD,p}$$

Pass Gate Resistance Calculation (Cont.)

- At this point, we devise an equivalent resistance for each transistor in this structure as follows

$$R_{eq,n} = \frac{V_{DD} - V_{out}}{I_{DS,n}}$$

$$R_{eq,p} = \frac{V_{DD} - V_{out}}{I_{SD,p}}$$

- The total equivalent resistance of the CMOS TG will be the parallel equivalent of these two resistances
- We will next calculate the equivalent resistance values for the three operating regions of the transmission gate

Pass Gate Resistance Calculation (Cont.)

- In region 1, $V_{out} < |V_{T,p}|$

- pMOS and nMOS transistors both in saturation

$$R_{eq,n} = \frac{2(V_{DD} - V_{out})}{k_n (V_{DD} - V_{out} - V_{T,n})^2} \quad R_{eq,p} = \frac{2(V_{DD} - V_{out})}{k_p (V_{DD} - |V_{T,p}|)^2}$$

- V_{SB} of NMOS transistor is equal to the output voltage, **while that for pMOS transistor is equal to zero**, therefore body bias for the nMOS transistor must be taken into account

- In region 2, $|V_{T,p}| < V_{out} < V_{DD} - V_{T,n}$

- pMOS in linear and nMOS in saturation

$$R_{eq,n} = \frac{2(V_{DD} - V_{out})}{k_n (V_{DD} - V_{out} - V_{T,n})^2} \quad R_{eq,p} = \frac{2}{k_p [2(V_{DD} - |V_{T,p}|) - (V_{DD} - V_{out})]}$$


- In region 3, the output voltage is $V_{out} > V_{DD} - V_{T,n}$

- pMOS in linear and nMOS in cutoff

$$R_{eq,n} = \infty \quad R_{eq,p} = \frac{2}{k_p [2(V_{DD} - |V_{T,p}|) - (V_{DD} - V_{out})]}$$

Pass Gate Resistance Calculation (Cont.)

 
- While individual $R_{eq,n}$ and $R_{eq,p}$ are strongly dependent on V_{out} , the total R_{eq} remains relatively constant, i.e., its value is almost independent of V_{out} (a quite desirable property)
- A CMOS pass gate which is turned on by a logic-high control signal can be replaced by its simple equivalent resistance for dynamic analysis




Equivalent resistance of the CMOS transmission gate

TG-based Cell Design

Two-input multiplexer


 


• XOR

 

Eight-transistor CMOS TG implementation


An arbitrary logic

 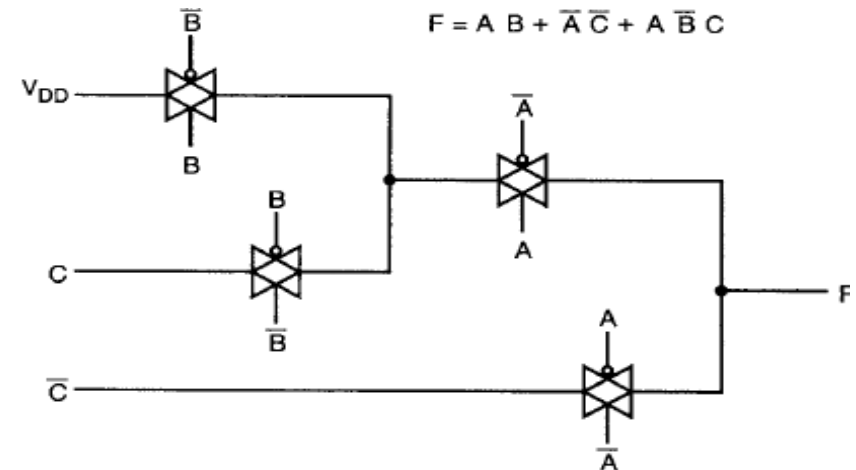


Six-transistor CMOS TG implementation

Complementary Pass-Transistor Logic

 - The complexity of full CMOS pass-gate logic circuits can be reduced by adopting **Complementary Pass-transistor Logic (CPL)**
- The idea is to use a purely nMOS pass-transistor network for the logic operations, instead of a CMOS TG network
- Every input signal and its complement must be provided





CPL NAND2 gate

 

CPL NOR2 gate

Full Scaling (Constant-Field Scaling)

Quantity	Before Scaling	After Scaling
Channel length	L	$L' = L/S$
Channel width	W	$W' = W/S$
Gate oxide thickness	t_{ox}	$t_{ox}' = t_{ox}/S$
Junction depth	x_j	$x_j' = x_j/S$
Power supply voltage	V_{DD}	$V_{DD}' = V_{DD}/S$
Threshold voltage	V_{T0}	$V_{T0}' = V_{T0}/S$
Doping densities	N_A & N_D	$N_A' = S.N_A$ & $N_D' = S.N_D$

  

Full Scaling (Cont.)

- I_D for linear and saturation modes:

$$\begin{aligned} I_D'(lin) &= \frac{k_n'}{2} \cdot [2 \cdot (V_{GS}' - V_T') V_{DS}' - V_{DS}'^2] \\ &= \frac{S \cdot k_n}{2} \cdot \frac{1}{S^2} \cdot [2 \cdot (V_{GS} - V_T) V_{DS} - V_{DS}^2] = \frac{I_D(lin)}{S} \end{aligned}$$

$$I_D'(sat) = \frac{k_n'}{2} \cdot (V_{GS}' - V_T')^2 = \frac{S \cdot k_n}{2} \cdot \frac{1}{S^2} \cdot (V_{GS} - V_T)^2 = \frac{I_D(sat)}{S}$$

- For power dissipation of the transistor, we obtain:

$$P' = I_D' \cdot V_{DS}' = \frac{1}{S^2} \cdot I_D \cdot V_{DS} = \frac{P}{S^2}$$

- Device area reduction by S^2 , so *power density* per unit area remains unchanged for the scaled device
- $C_g = WLC_{ox}$ scales down by S , therefore faster charge-up charge-down for the scaled device
 - Reduced dimensions would result in reduction of various parasitic caps and resistances

Technology Trend

- <http://www.itrs.net/Links/2011ITRS/Home2011.htm>